

11-19-2015

## 20. Alternating Currents

Gerhard Müller  
University of Rhode Island, gmuller@uri.edu

Follow this and additional works at: [https://digitalcommons.uri.edu/elementary\\_physics\\_2](https://digitalcommons.uri.edu/elementary_physics_2)

### Abstract

Lecture slides 20 for Elementary Physics II (PHY 204), taught by Gerhard Müller at the University of Rhode Island.

Some of the slides contain figures from the textbook, Paul A. Tipler and Gene Mosca. *Physics for Scientists and Engineers*, 5<sup>th</sup>/6<sup>th</sup> editions. The copyright to these figures is owned by W.H. Freeman. We acknowledge permission from W.H. Freeman to use them on this course web page. The textbook figures are not to be used or copied for any purpose outside this class without direct permission from W.H. Freeman.

---

### Recommended Citation

Müller, Gerhard, "20. Alternating Currents" (2015). *PHY 204: Elementary Physics II (2015)*. Paper 4. [https://digitalcommons.uri.edu/elementary\\_physics\\_2/4](https://digitalcommons.uri.edu/elementary_physics_2/4)



This Course Material is brought to you for free and open access by the Physics Open Educational Resources at DigitalCommons@URI. It has been accepted for inclusion in PHY 204: Elementary Physics II (2015) by an authorized administrator of DigitalCommons@URI. For more information, please contact [digitalcommons-group@uri.edu](mailto:digitalcommons-group@uri.edu).
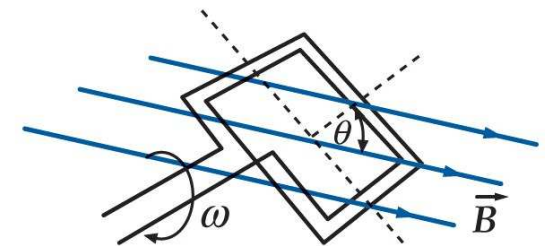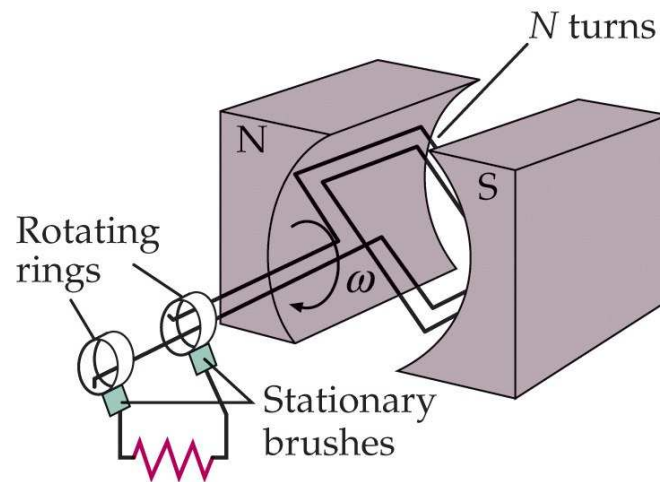
# Alternating Current Generator



Coil of  $N$  turns and cross-sectional area  $A$  rotating with angular frequency  $\omega$  in uniform magnetic field  $\vec{B}$ .

- Angle between area vector and magnetic field vector:  $\theta = \omega t$ .
- Flux through coil:  $\Phi_B = NBA \cos(\omega t)$ .
- Induced EMF:  $\mathcal{E} = -\frac{d\Phi_B}{dt} = \mathcal{E}_{max} \sin(\omega t)$  with amplitude  $\mathcal{E}_{max} = NBA\omega$ .
- U.S. household outlet values:
  - $\mathcal{E}_{max} = 120V\sqrt{2} \simeq 170V$
  - $f = 60\text{Hz}$ ,  $\omega = 2\pi f \simeq 377\text{rad/s}$ .



# Single Device in AC Circuit: Resistor



Voltage of ac source :  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$




Current through device:  $I = I_{max} \cos(\omega t - \delta)$

## Resistor

$$V_R = RI = \mathcal{E}_{max} \cos \omega t \Rightarrow I = \frac{\mathcal{E}_{max}}{R} \cos \omega t$$

amplitude:  $I_{max} = \frac{\mathcal{E}_{max}}{R}$ , phase angle:  $\delta = 0$

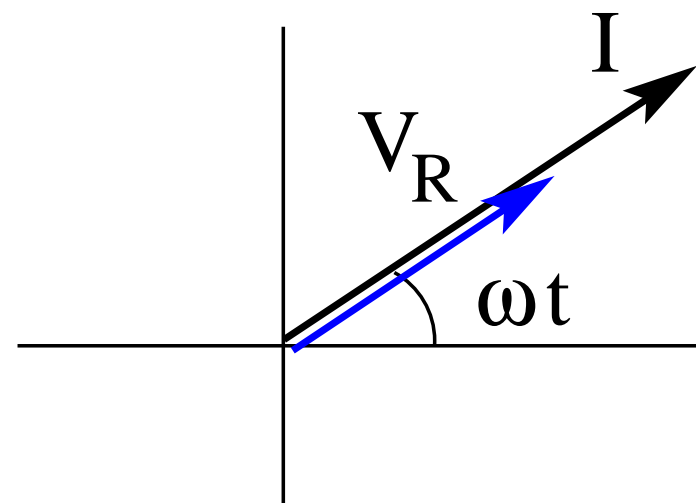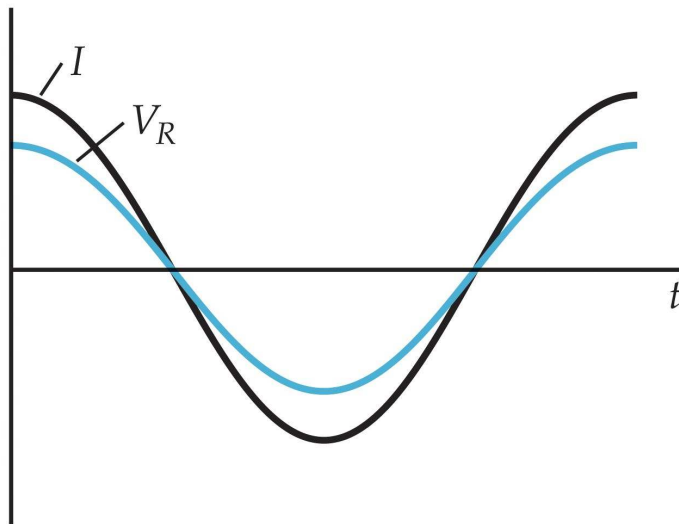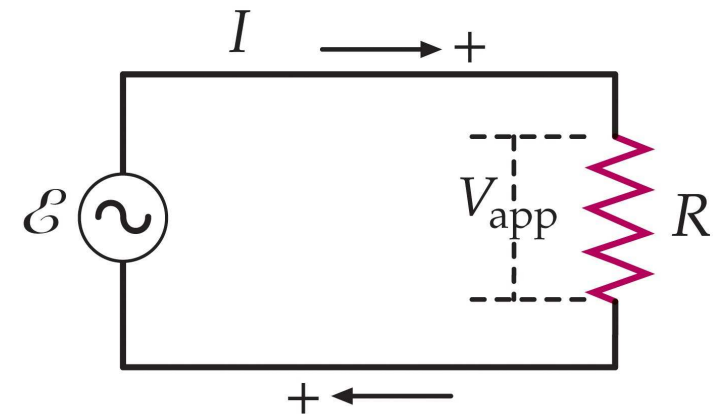impedance:  $X_R \equiv \frac{\mathcal{E}_{max}}{I_{max}} = R$  (resistance)



# Single Device in AC Circuit: Inductor



Voltage of ac source :  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$




Current through device:  $I = I_{max} \cos(\omega t - \delta)$

## Inductor

$$V_L = L \frac{dI}{dt} = \mathcal{E}_{max} \cos \omega t \Rightarrow I = \frac{\mathcal{E}_{max}}{\omega L} \sin(\omega t)$$

amplitude:  $I_{max} = \frac{\mathcal{E}_{max}}{\omega L}$ , phase angle:  $\delta = \frac{\pi}{2}$

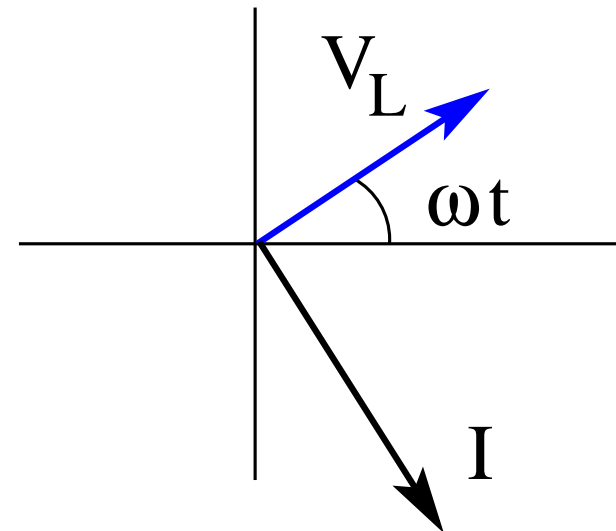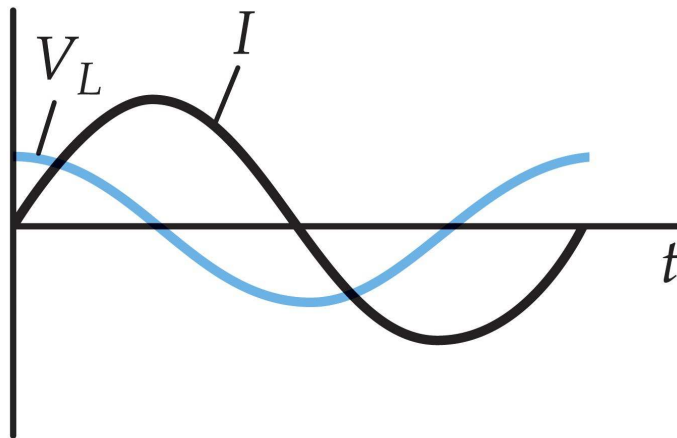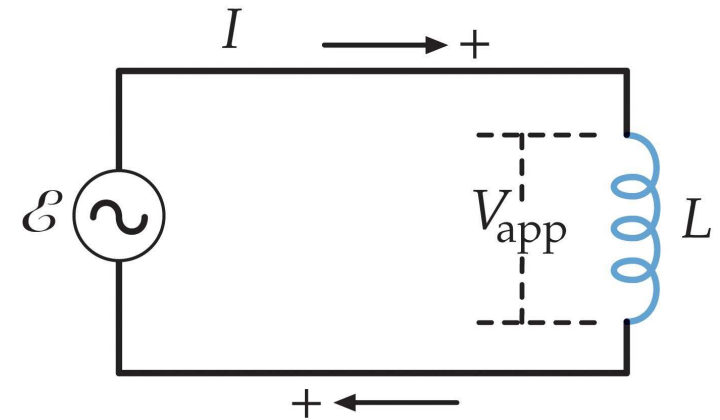impedance:  $X_L \equiv \frac{\mathcal{E}_{max}}{I_{max}} = \omega L$  (inductive reactance)



# Single Device in AC Circuit: Capacitor



Voltage of ac source :  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$




Current through device:  $I = I_{max} \cos(\omega t - \delta)$

## Capacitor

$$V_C = \frac{Q}{C} = \mathcal{E}_{max} \cos \omega t \Rightarrow I = \frac{dQ}{dt} = -\omega C \mathcal{E}_{max} \sin(\omega t)$$

amplitude:  $I_{max} = \omega C \mathcal{E}_{max}$ , phase angle:  $\delta = -\frac{\pi}{2}$

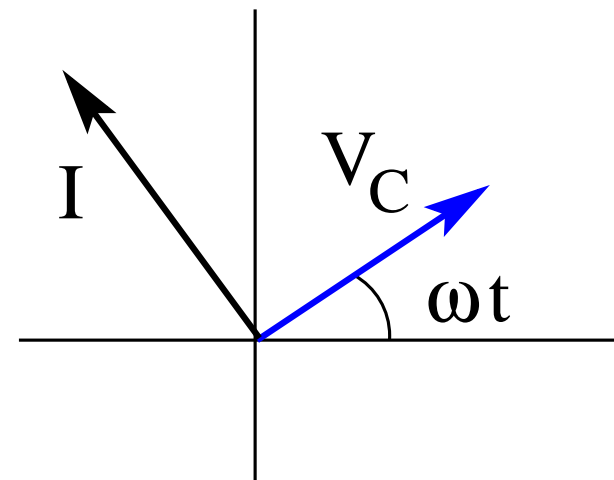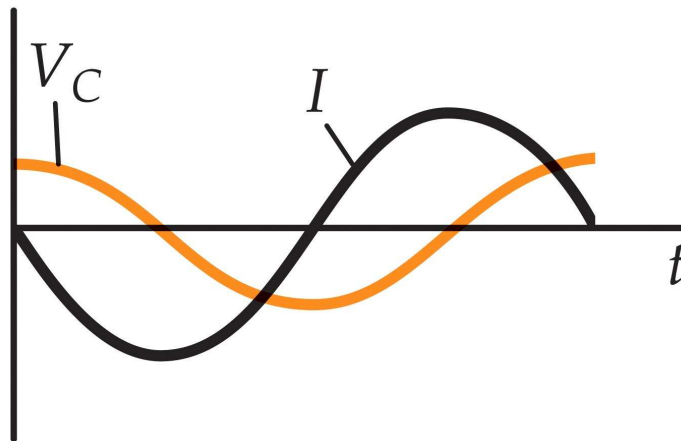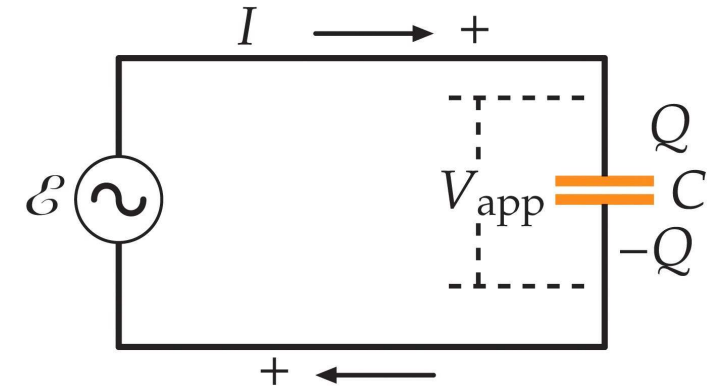impedance:  $X_C \equiv \frac{\mathcal{E}_{max}}{I_{max}} = \frac{1}{\omega C}$  (capacitive reactance)






# Single Device in AC Circuit: Application (1)



The ac voltage source  $\mathcal{E} = \mathcal{E}_{max} \sin \omega t$  has an amplitude of  $\mathcal{E}_{max} = 24\text{V}$  and an angular frequency of  $\omega = 10\text{rad/s}$ .

In each of the three circuits, find

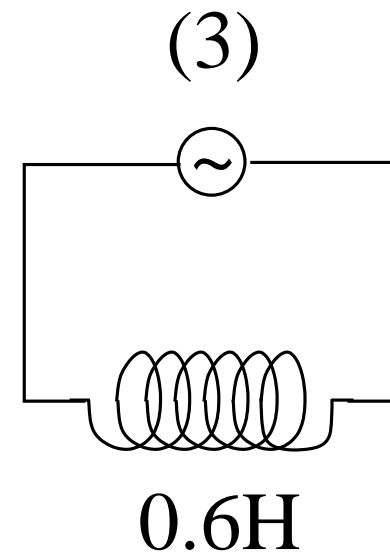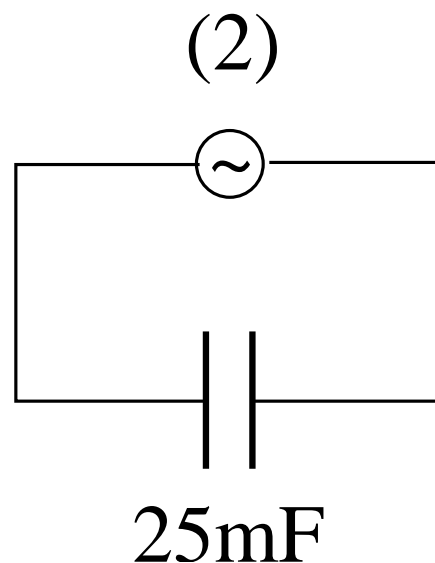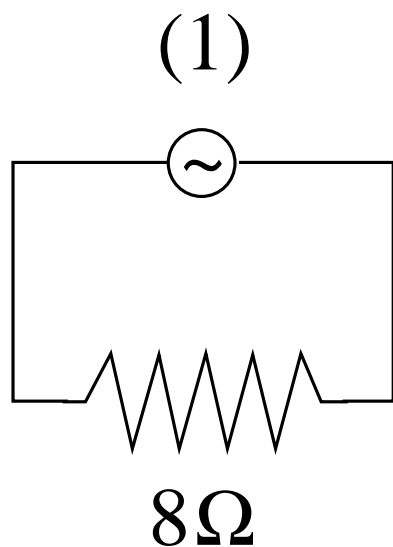- (a) the current amplitude  $I_{max}$ ,
- (b) the current  $I$  at time  $t = 1\text{s}$ .



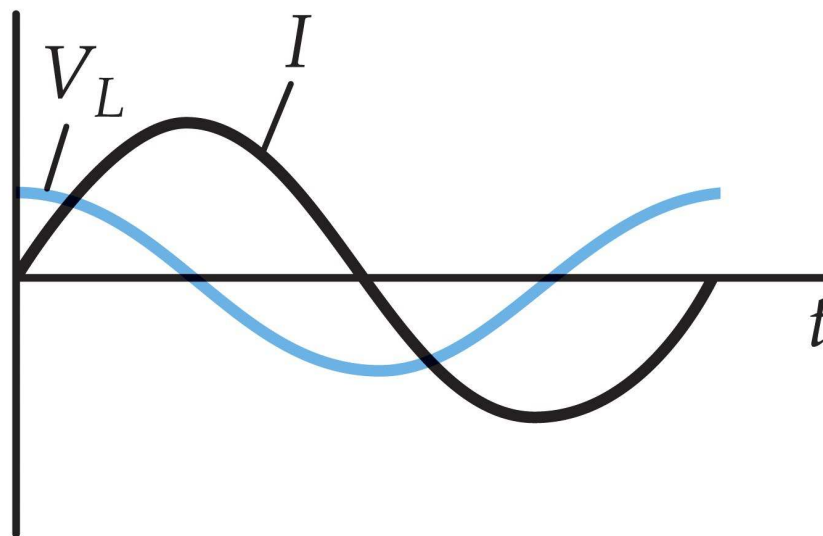
## Single Device in AC Circuit: Application (2)



Consider an ac generator  $\mathcal{E}(t) = \mathcal{E}_{max} \cos(\omega t)$ ,  $\mathcal{E}_{max} = 25\text{V}$ ,  $\omega = 377\text{rad/s}$  connected to an inductor with inductance  $L = 12.7\text{H}$ .

- Find the maximum value of the current.
- Find the current when the emf is zero and decreasing.
- Find the current when the emf is  $-12.5\text{V}$  and decreasing.
- Find the power supplied by the generator at the instant described in (c).




## Single Device in AC Circuit: Application (3)



Consider an ac generator  $\mathcal{E}(t) = \mathcal{E}_{max} \cos(\omega t)$ ,  $\mathcal{E}_{max} = 25\text{V}$ ,  $\omega = 377\text{rad/s}$  connected to a capacitor with capacitance  $C = 4.15\mu\text{F}$ .

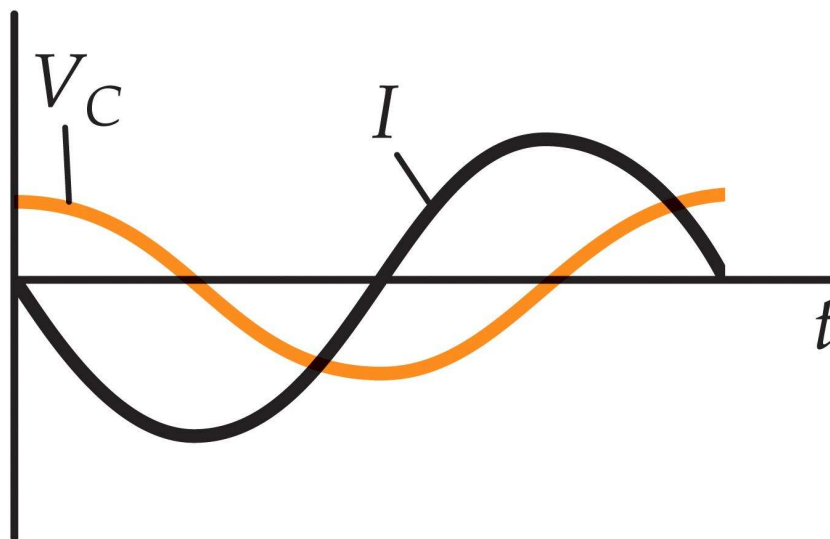- (a) Find the maximum value of the current.
- (b) Find the current when the emf is zero and decreasing.
- (c) Find the current when the emf is  $-12.5\text{V}$  and increasing.
- (d) Find the power supplied by the generator at the instant described in (c).





# RLC Series Circuit (1)



Applied alternating voltage:  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$

Resulting alternating current:  $I = I_{max} \cos(\omega t - \delta)$


Goals:

- Find  $I_{max}, \delta$  for given  $\mathcal{E}_{max}, \omega$ .
- Find voltages  $V_R, V_L, V_C$  across devices.

Loop rule:  $\mathcal{E} - V_R - V_C - V_L = 0$

Note:

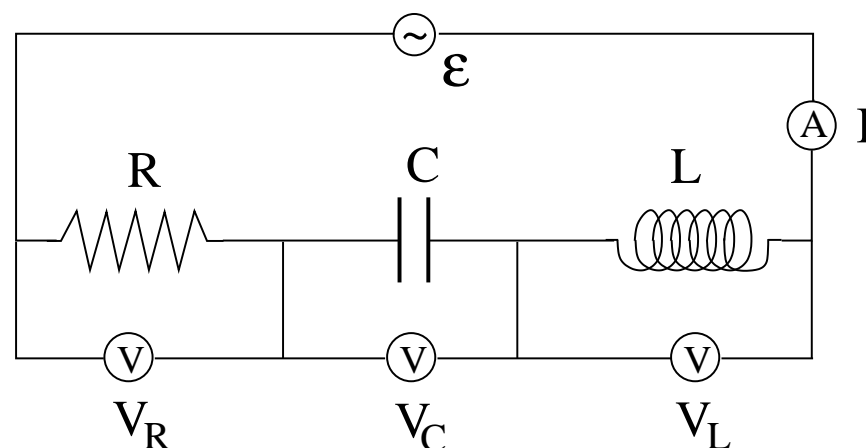- All voltages are time-dependent.
- In general, all voltages have a different phase.
- $V_R$  has the same phase as  $I$ .




## RLC Series Circuit (2)



Phasor diagram (for  $\omega t = \delta$ ):

Voltage amplitudes:

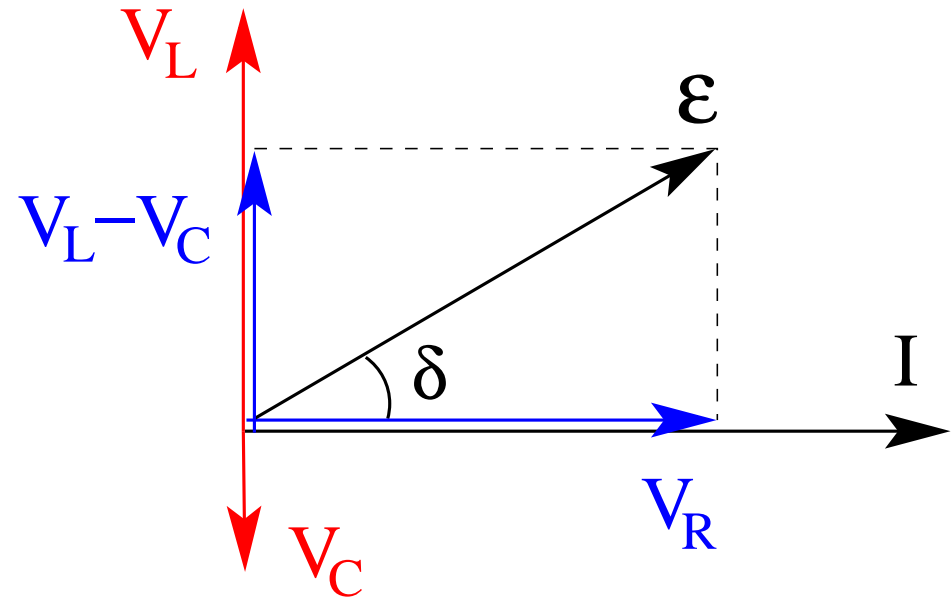- $V_{R,max} = I_{max}X_R = I_{max}R$
- $V_{L,max} = I_{max}X_L = I_{max}\omega L$
- $V_{C,max} = I_{max}X_C = \frac{I_{max}}{\omega C}$



Relation between  $\mathcal{E}_{max}$  and  $I_{max}$  from geometry:

$$\begin{aligned}\mathcal{E}_{max}^2 &= V_{R,max}^2 + (V_{L,max} - V_{C,max})^2 \\ &= I_{max}^2 \left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]\end{aligned}$$


# RLC Series Circuit (3)



Impedance:  $Z \equiv \frac{\mathcal{E}_{max}}{I_{max}} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$

Current amplitude and phase angle:

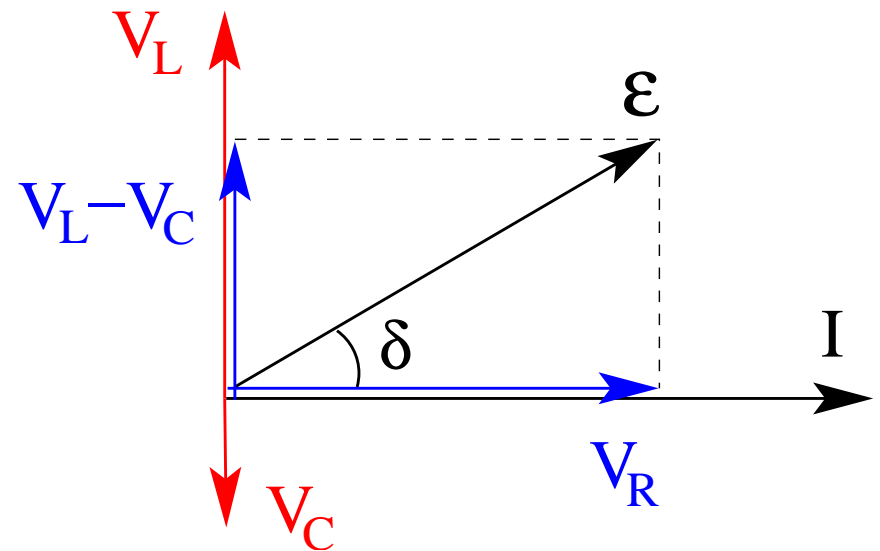- $I_{max} = \frac{\mathcal{E}_{max}}{Z} = \frac{\mathcal{E}_{max}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$
- $\tan \delta = \frac{V_{L,max} - V_{C,max}}{V_{R,max}} = \frac{\omega L - 1/\omega C}{R}$



Voltages across devices:

- $V_R = RI = RI_{max} \cos(\omega t - \delta) = V_{R,max} \cos(\omega t - \delta)$
- $V_L = L \frac{dI}{dt} = -\omega LI_{max} \sin(\omega t - \delta) = V_{L,max} \cos\left(\omega t - \delta + \frac{\pi}{2}\right)$
- $V_C = \frac{1}{C} \int I dt = \frac{I_{max}}{\omega C} \sin(\omega t - \delta) = V_{C,max} \cos\left(\omega t - \delta - \frac{\pi}{2}\right)$


# AC Circuit Application (1)



In this  $RLC$  circuit, the voltage amplitude is  $\mathcal{E}_{max} = 100\text{V}$ .

Find the impedance  $Z$ , the current amplitude  $I_{max}$ , and the voltage amplitudes  $V_R, V_C, V_L, V_{LC}$

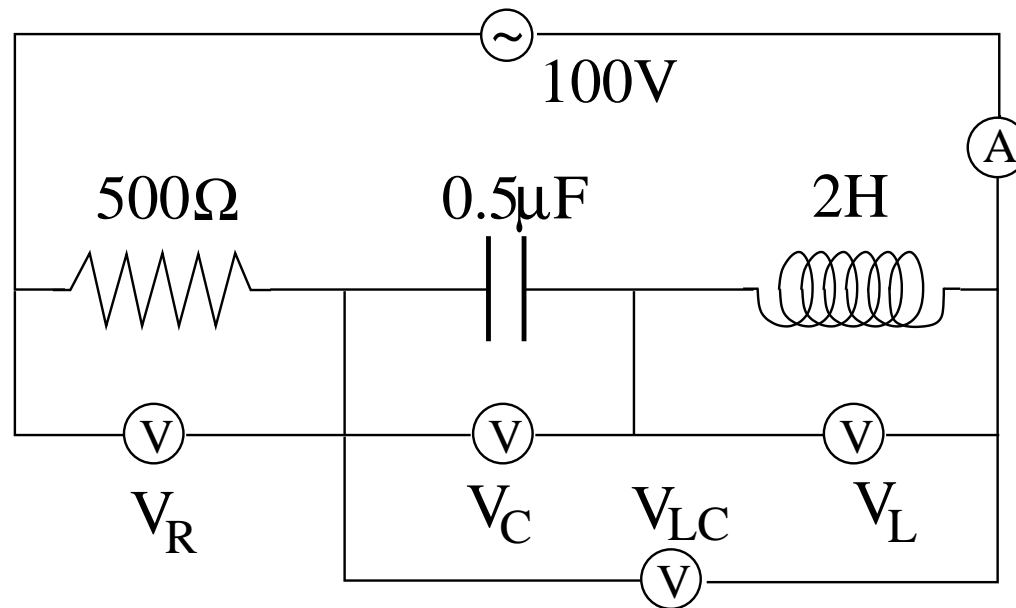- (a) for angular frequency is  $\omega = 1000\text{rad/s}$ ,
- (b) for angular frequency is  $\omega = 500\text{rad/s}$ .



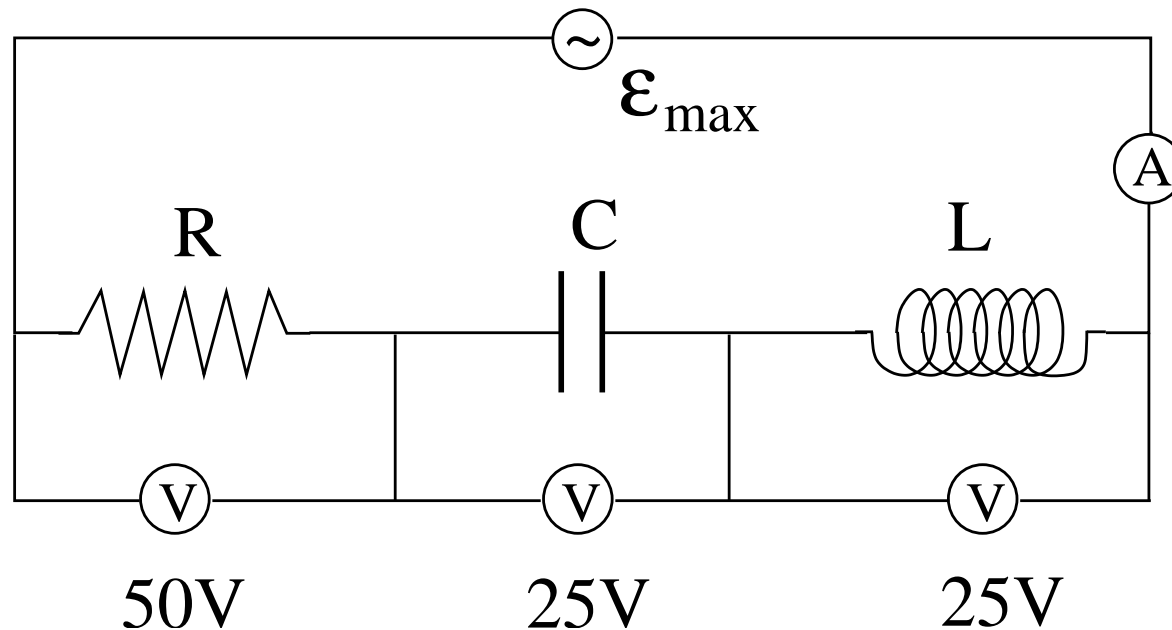
## AC Circuit Application (2)



In this  $RLC$  circuit, we know the voltage amplitudes  $V_R, V_C, V_L$  across each device, the current amplitude  $I_{max} = 5A$ , and the angular frequency  $\omega = 2\text{rad/s}$ .

- Find the device properties  $R, C, L$  and the voltage amplitude  $\mathcal{E}_{max}$  of the ac source.



# Impedances: RLC in Series (1)





$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

resonance at  $\omega_0 = \frac{1}{\sqrt{LC}}$

limit  $R \rightarrow 0$

$$Z = \left| \omega L - \frac{1}{\omega C} \right|$$

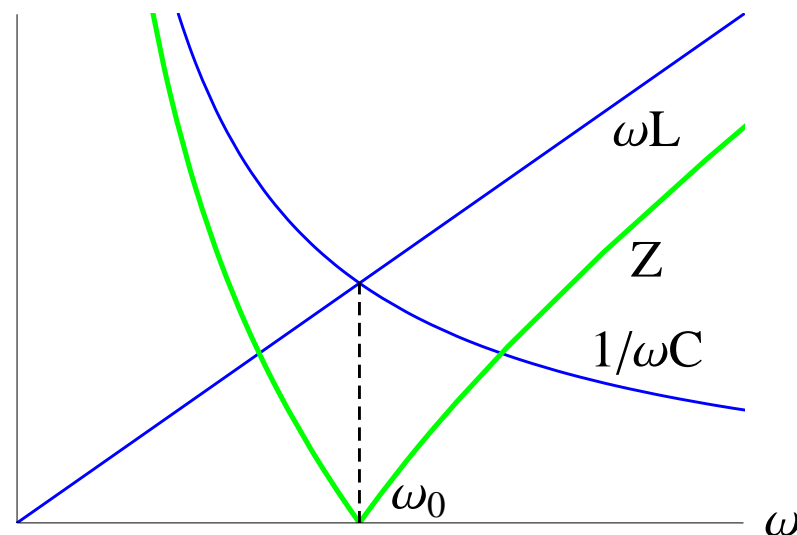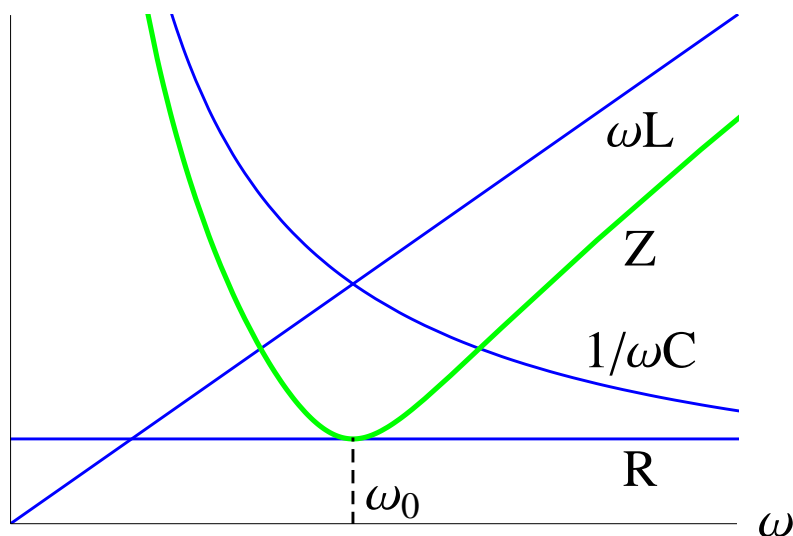


# Impedances: RLC in Series (2)




limit  $C \rightarrow \infty$

$$Z = \sqrt{R^2 + (\omega L)^2}$$


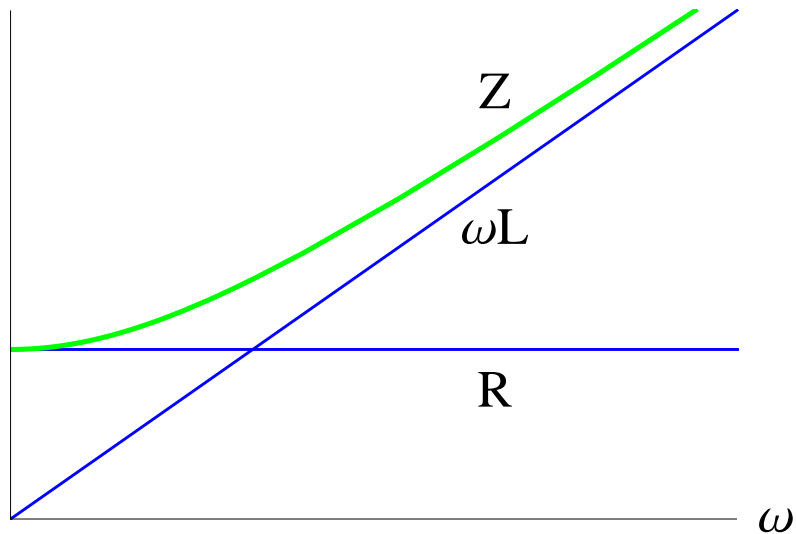


limit  $L \rightarrow 0$
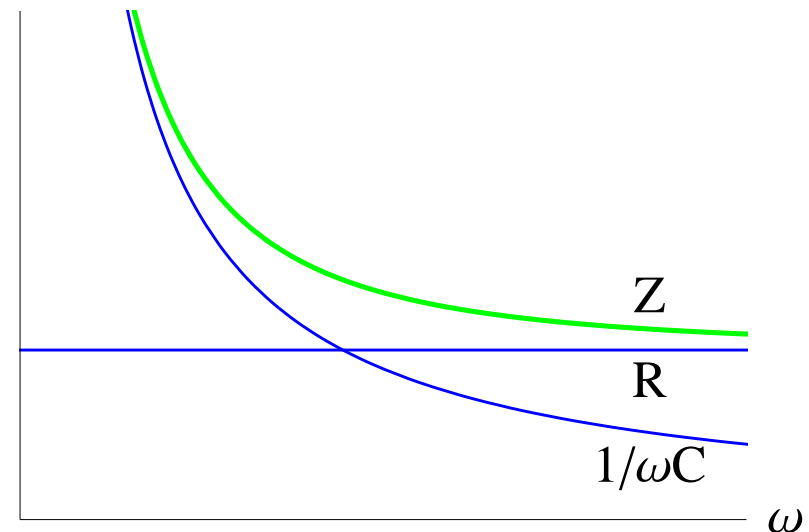
$$Z = \sqrt{R^2 + \frac{1}{(\omega C)^2}}$$



# Filters

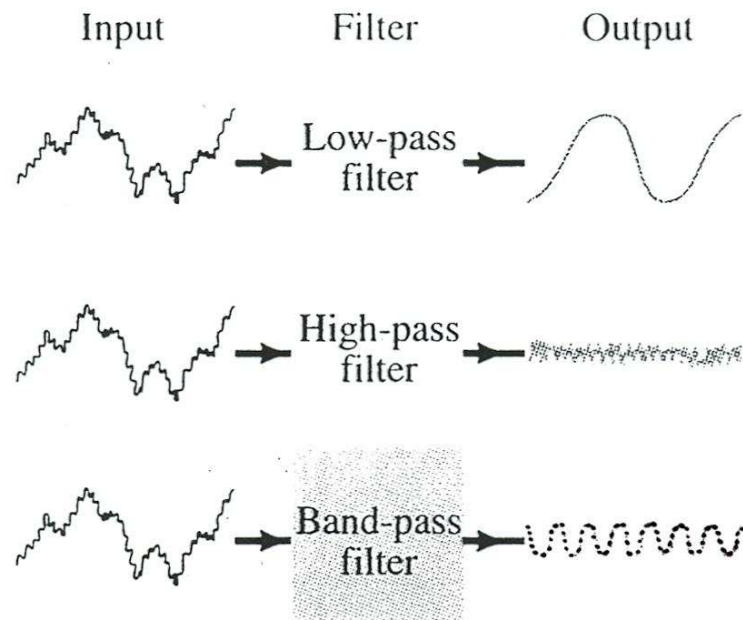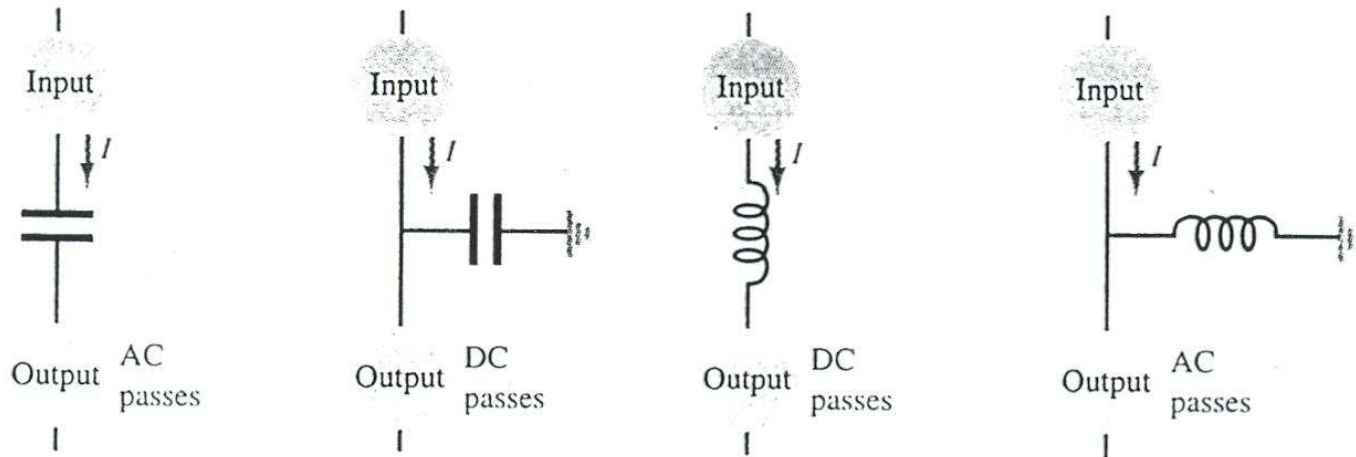



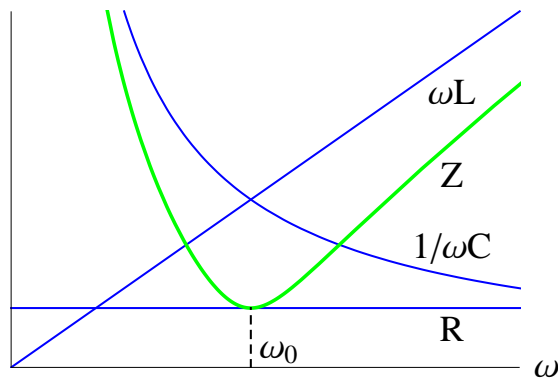
# RLC Series Resonance (1)




impedance

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$




current
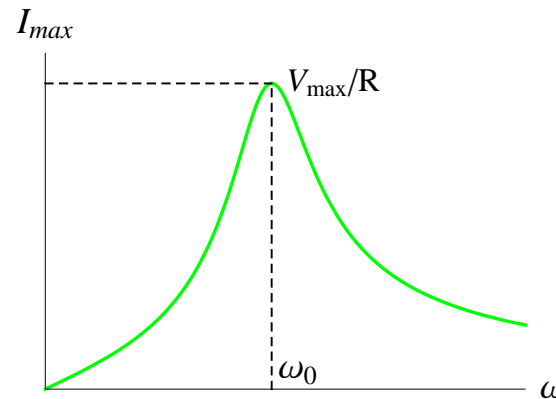
$$I_{max} = \frac{V_{max}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$



phase angle
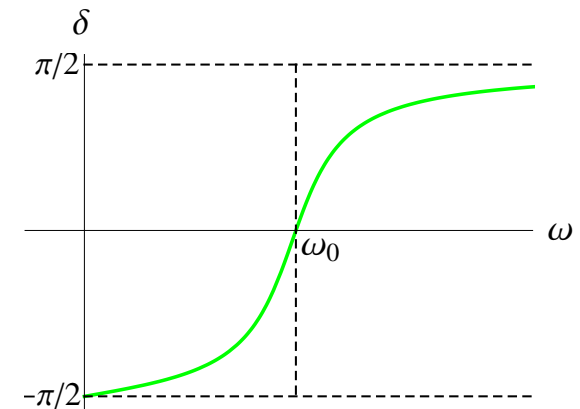
$$\delta = \frac{\omega L - 1/\omega C}{R}$$



resonance angular frequency:


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

# RLC Series Resonance (2)




resistor

$$V_R^{max} = I_{max} R$$

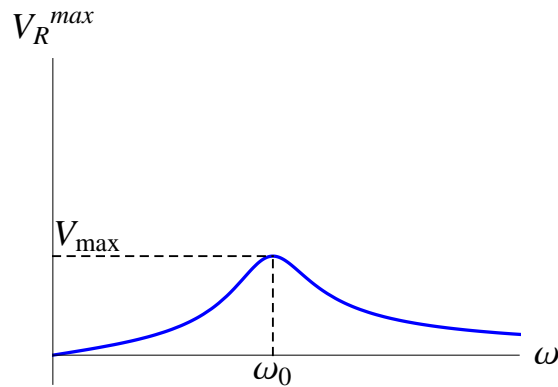


inductor

$$V_L^{max} = I_{max} \omega L$$

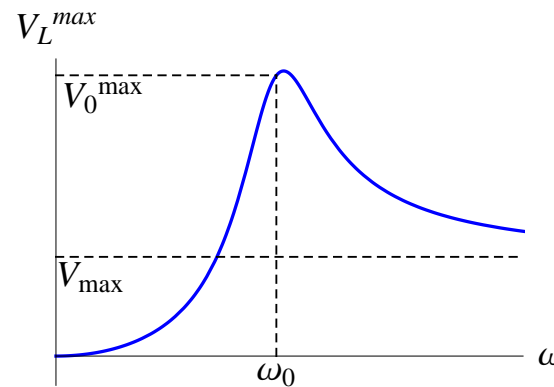

capacitor

$$V_C^{max} = I_{max} / \omega C$$

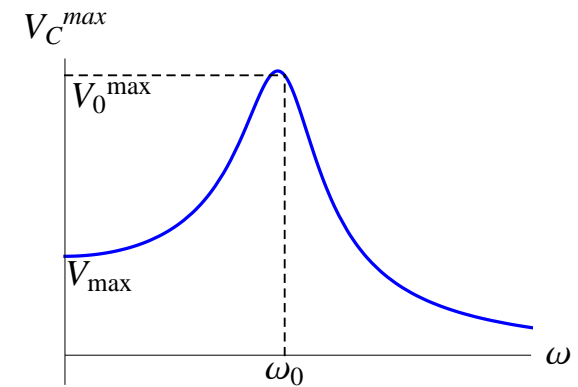

- relaxation times:  $\tau_{RC} = RC$ ,  $\tau_{RL} = L/R$

- angular frequencies:  $\omega_L = \frac{\omega_0}{\sqrt{1 - (\omega_0 \tau_{RC})^2/2}}$ ,  $\omega_C = \omega_0 \sqrt{1 - (\omega_0 \tau_{RC})^2/2}$

- voltages:  $V_0^{max} = V_{max} \omega_0 \tau_{RL}$ ,  $V_L^{max}(\omega_L) = V_C^{max}(\omega_C) = \frac{V_0^{max}}{\sqrt{1 - (\omega_0 \tau_{RC})^2/4}}$

# RLC Parallel Circuit (1)



Applied alternating voltage:  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$

Resulting alternating current:  $I = I_{max} \cos(\omega t - \delta)$


Goals:

- Find  $I_{max}, \delta$  for given  $\mathcal{E}_{max}, \omega$ .
- Find currents  $I_R, I_L, I_C$  through devices.

Junction rule:  $I = I_R + I_L + I_C$

Note:

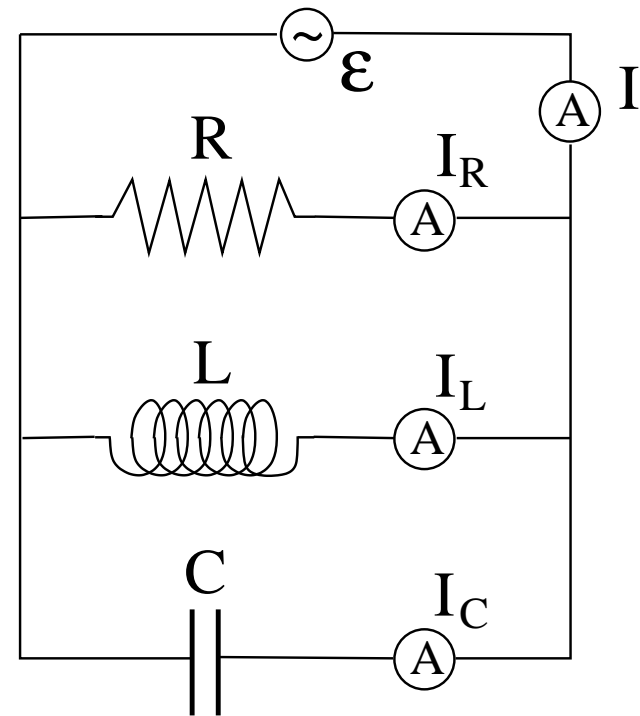- All currents are time-dependent.
- In general, each current has a different phase
- $I_R$  has the same phase as  $\mathcal{E}$ .




## RLC Parallel Circuit (2)



Phasor diagram (for  $\omega t = \delta$ ):

Current amplitudes:

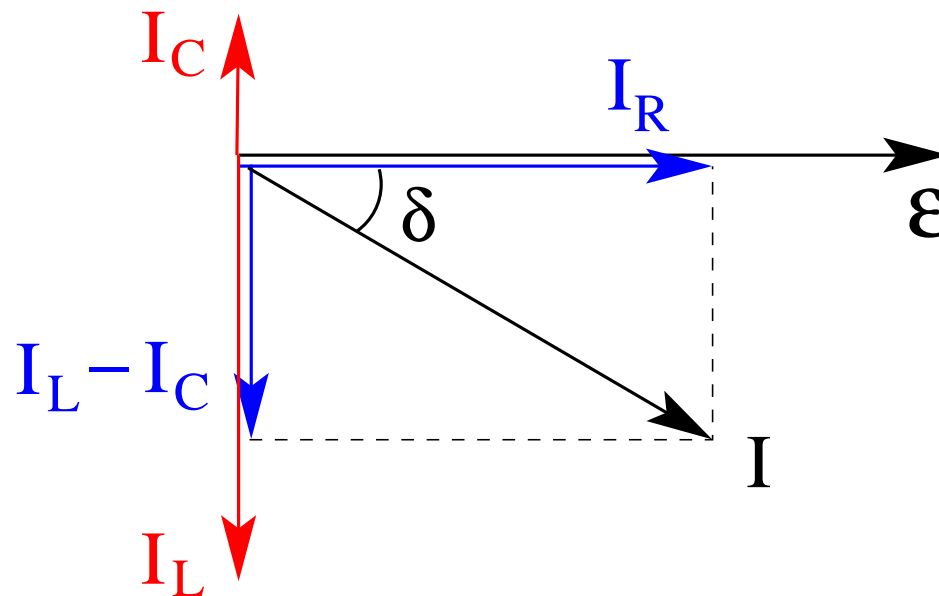- $I_{R,max} = \frac{\mathcal{E}_{max}}{X_R} = \frac{\mathcal{E}_{max}}{R}$
- $I_{L,max} = \frac{\mathcal{E}_{max}}{X_L} = \frac{\mathcal{E}_{max}}{\omega L}$
- $I_{C,max} = \frac{\mathcal{E}_{max}}{X_C} = \mathcal{E}_{max}\omega C$



Relation between  $\mathcal{E}_{max}$  and  $I_{max}$  from geometry:

$$\begin{aligned} I_{max}^2 &= I_{R,max}^2 + (I_{L,max} - I_{C,max})^2 \\ &= \mathcal{E}_{max}^2 \left[ \frac{1}{R^2} + \left( \frac{1}{\omega L} - \omega C \right)^2 \right] \end{aligned}$$


# RLC Parallel Circuit (3)



Impedance:  $\frac{1}{Z} \equiv \frac{I_{max}}{\mathcal{E}_{max}} = \sqrt{\frac{1}{R^2} + \left(\frac{1}{\omega L} - \omega C\right)^2}$

Current amplitude and phase angle:

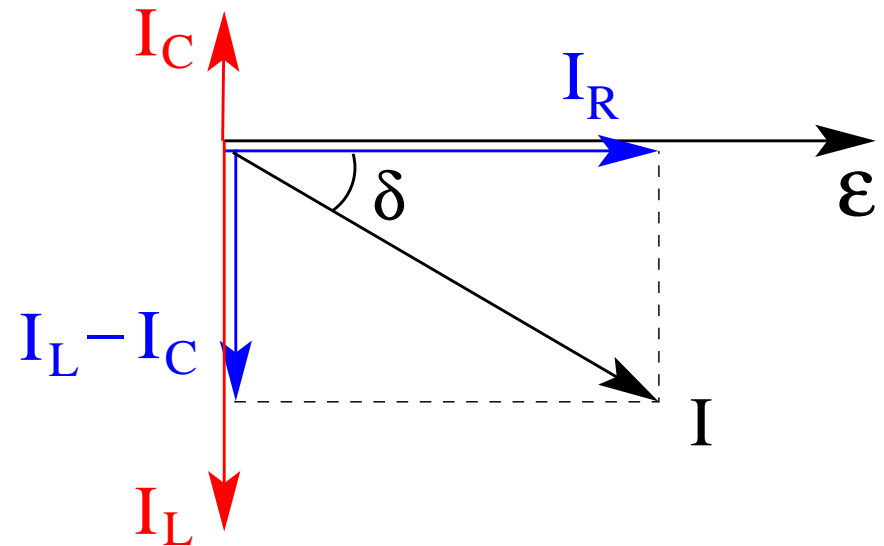- $I_{max} = \frac{\mathcal{E}_{max}}{Z} = \mathcal{E}_{max} \sqrt{\frac{1}{R^2} + \left(\frac{1}{\omega L} - \omega C\right)^2}$
- $\tan \delta = \frac{I_{L,max} - I_{C,max}}{I_{R,max}} = \frac{1/\omega L - \omega C}{1/R}$



Currents through devices:


- $I_R = \frac{\mathcal{E}}{R} = \frac{\mathcal{E}_{max}}{R} \cos(\omega t) = I_{R,max} \cos(\omega t)$
- $I_L = \frac{1}{L} \int \mathcal{E} dt = \frac{\mathcal{E}_{max}}{\omega L} \sin(\omega t) = I_{L,max} \cos\left(\omega t - \frac{\pi}{2}\right)$
- $I_C = C \frac{d\mathcal{E}}{dt} = -\omega C \mathcal{E}_{max} \sin(\omega t) = I_{C,max} \cos\left(\omega t + \frac{\pi}{2}\right)$

## AC Circuit Application (3)



Find the current amplitudes  $I_1, I_2, I_3$

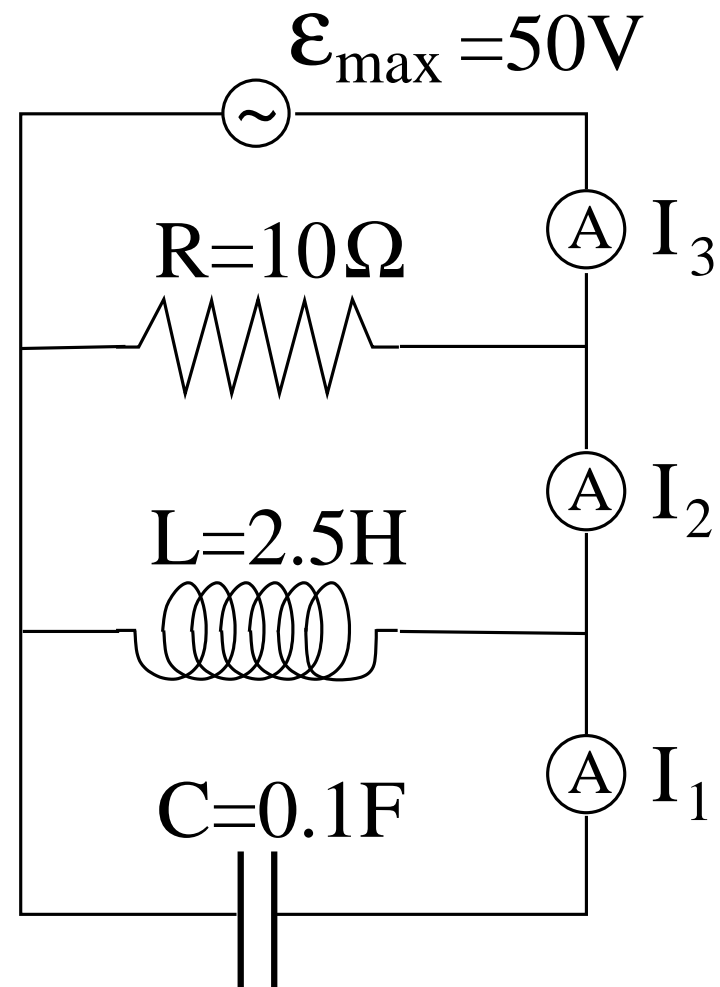
- (a) for angular frequency  $\omega = 2\text{rad/s}$ ,
- (b) for angular frequency  $\omega = 4\text{rad/s}$ .


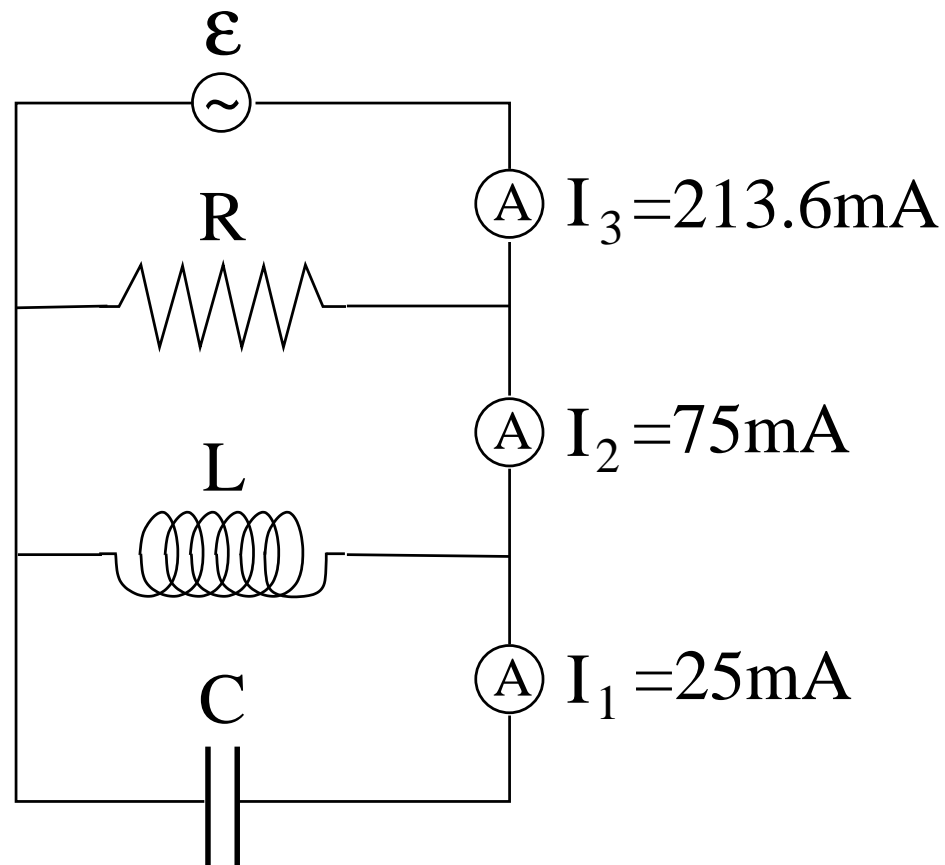
## AC Circuit Application (4)



Given the current amplitudes  $I_1, I_2, I_3$  through the three branches of this  $RLC$  circuit, and given the amplitude  $\mathcal{E}_{max} = 100\text{V}$  and angular frequency  $\omega = 500\text{rad/s}$  of the ac source, find the device properties  $R, L, C$ .



# Impedances: RLC in Parallel (1)





$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

resonance at  $\omega_0 = \frac{1}{\sqrt{LC}}$

limit  $R \rightarrow \infty$

$$\frac{1}{Z} = \left| \omega C - \frac{1}{\omega L} \right|$$

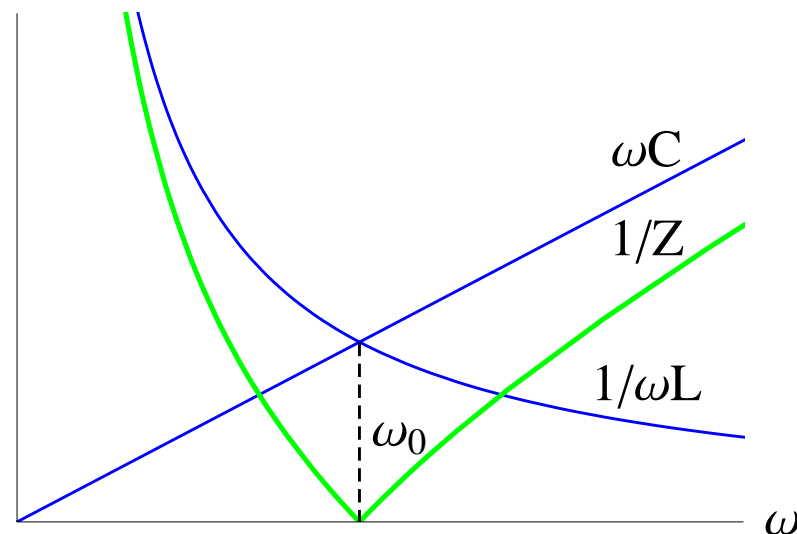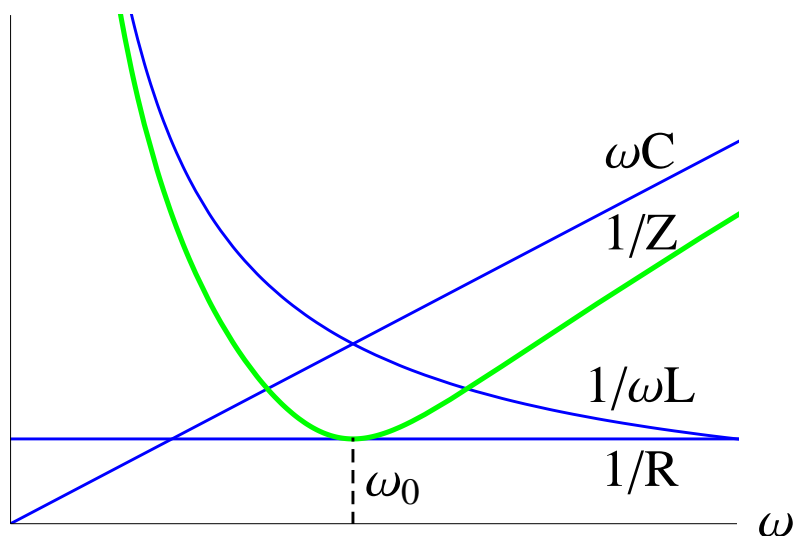



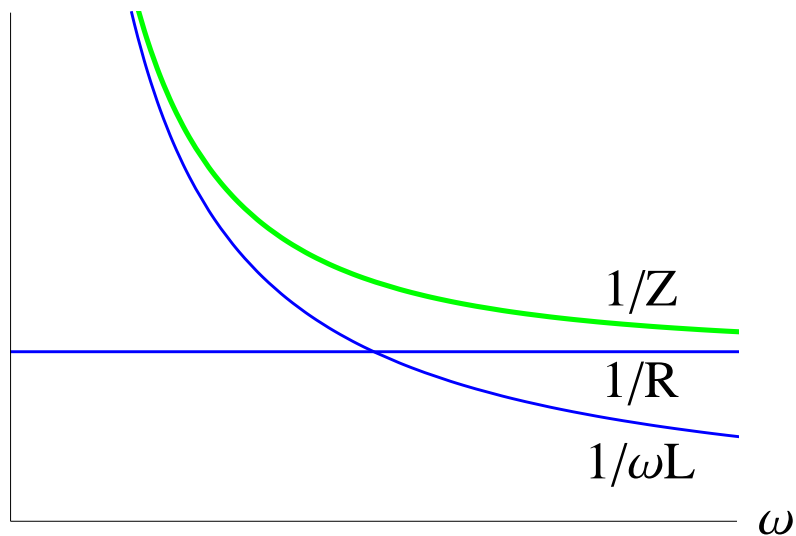
# Impedances: RLC in Parallel (2)




limit  $C \rightarrow 0$

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \frac{1}{(\omega L)^2}}$$



limit  $L \rightarrow \infty$
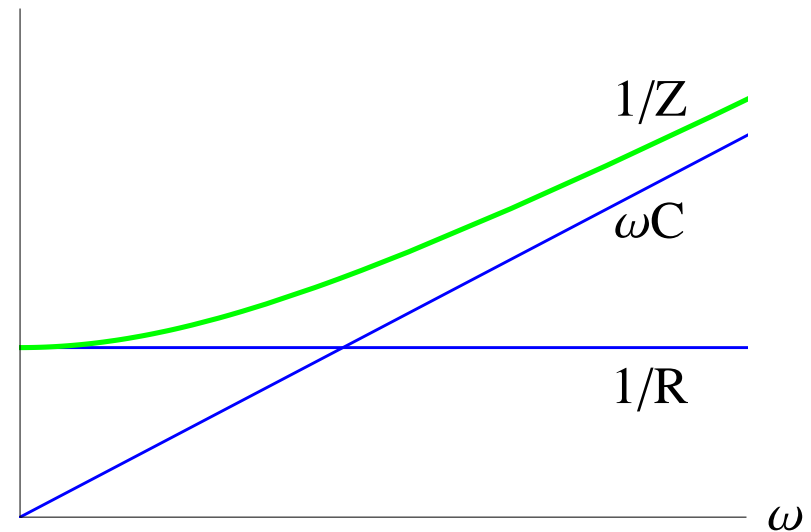
$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + (\omega C)^2}$$



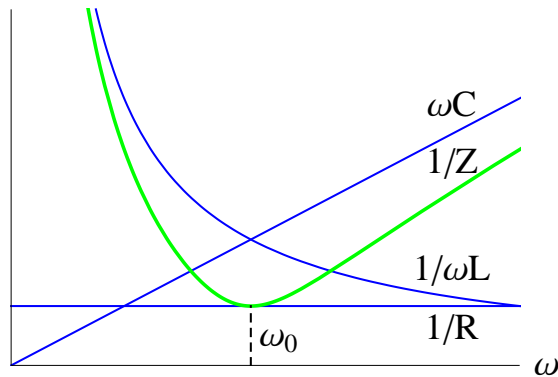
# RLC Parallel Resonance (1)




impedance

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}$$




current

$$I_{max} = \frac{V_{max}}{Z}$$

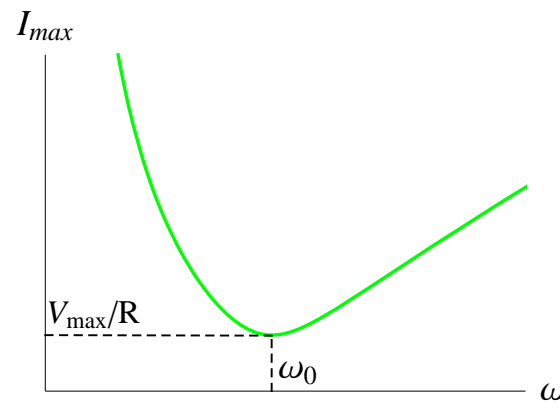

phase angle
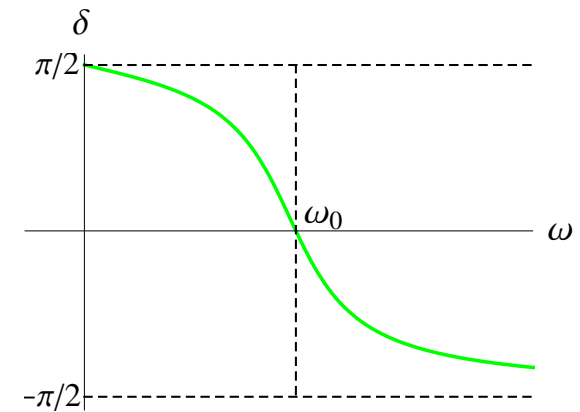
$$\delta = \frac{1/\omega L - \omega C}{1/R}$$



resonance angular frequency:


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

# RLC Parallel Resonance (2)




resistor

$$I_R^{max} = V_{max}/R$$

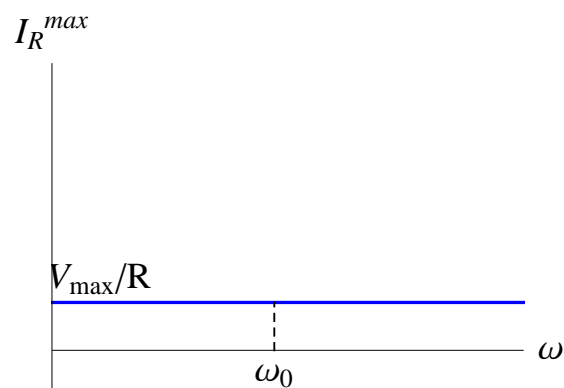


inductor

$$I_L^{max} = V_{max}/\omega L$$

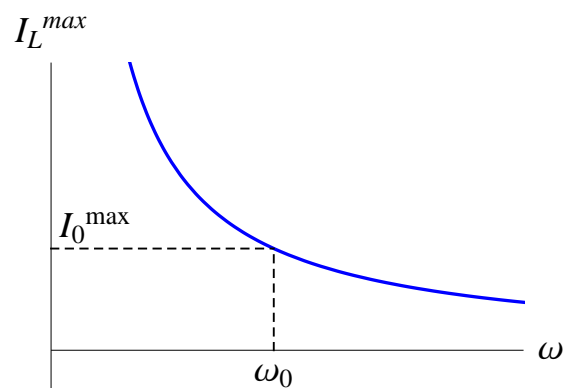

capacitor

$$I_C^{max} = V_{max} \omega C$$

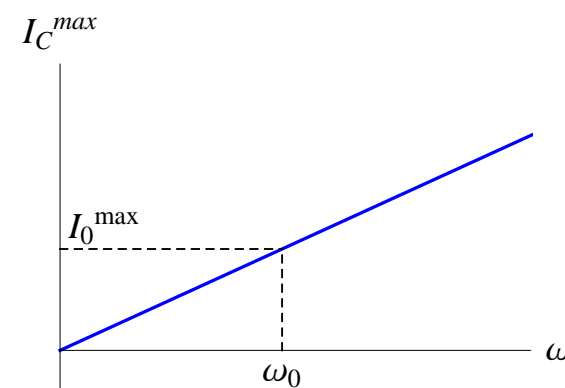

currents at resonance:

$$I_R^{max} = \frac{V_{max}}{R}, \quad I_L^{max} = I_C^{max} = I_0^{max} = V_{max} \sqrt{\frac{C}{L}}$$

# Power in AC Circuits



Voltage of ac source:  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$

Current through circuit:  $I = I_{max} \cos(\omega t - \delta)$

Instantaneous power supplied:  $P(t) = \mathcal{E}(t)I(t) = [\mathcal{E}_{max} \cos \omega t][I_{max} \cos(\omega t - \delta)]$



Use  $\cos(\omega t - \delta) = \cos \omega t \cos \delta + \sin \omega t \sin \delta$

$$\Rightarrow P(t) = \mathcal{E}_{max} I_{max} [\cos^2 \omega t \cos \delta + \cos \omega t \sin \omega t \sin \delta]$$

Time averages:  $[\cos^2 \omega t]_{AV} = \frac{1}{2}$ ,  $[\cos \omega t \sin \omega t]_{AV} = 0$

Average power supplied by source:  $P_{AV} = \frac{1}{2} \mathcal{E}_{max} I_{max} \cos \delta = \mathcal{E}_{rms} I_{rms} \cos \delta$

Power factor:  $\cos \delta$

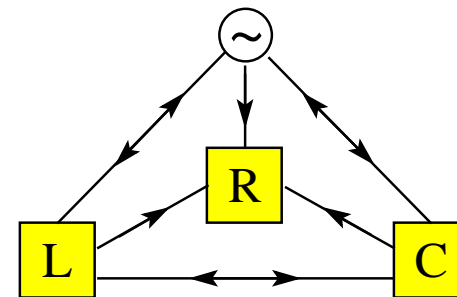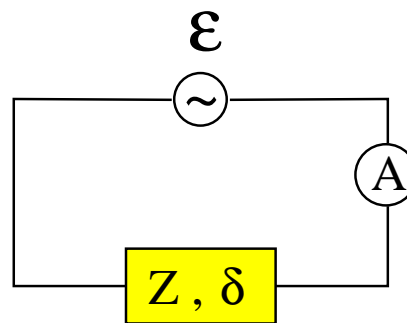

# Transformer



- Primary winding:  $N_1$  turns


$$V_1(t) = V_1^{(rms)} \cos(\omega t), \quad I_1(t) = I_1^{(rms)} \cos(\omega t - \delta_1)$$

- Secondary winding:  $N_2$  turns

$$V_2(t) = V_2^{(rms)} \cos(\omega t), \quad I_2(t) = I_2^{(rms)} \cos(\omega t - \delta_2)$$

- Voltage amplitude ratio:  $\frac{V_1^{(rms)}}{V_2^{(rms)}} = \frac{N_1}{N_2}$




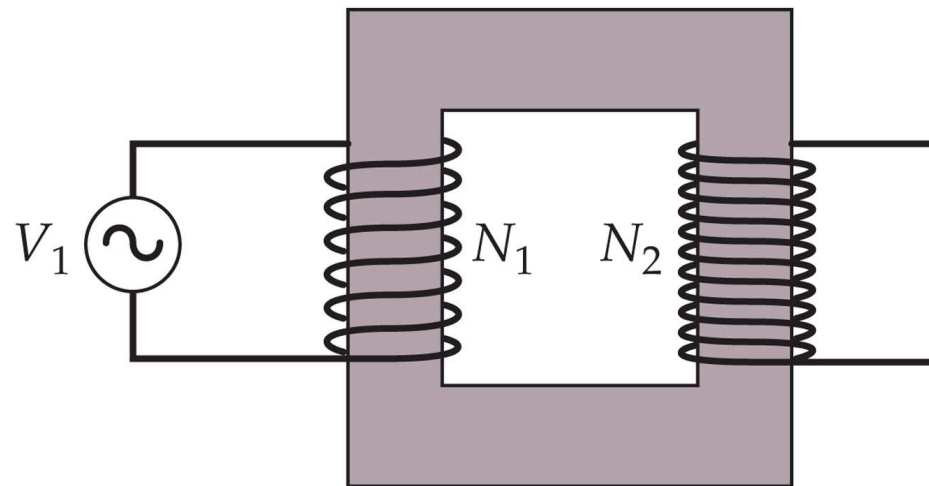
- Power transfer:  $V_1^{(rms)} I_1^{(rms)} \cos \delta_1 = V_2^{(rms)} I_2^{(rms)} \cos \delta_2$


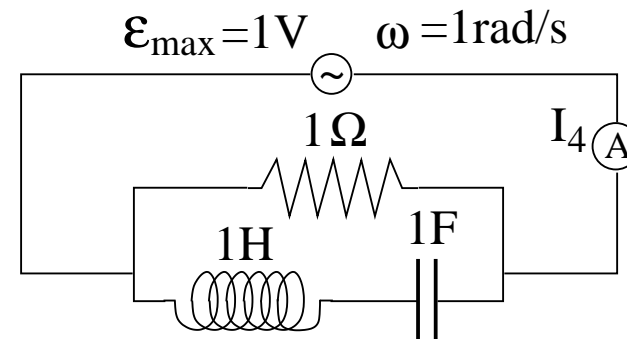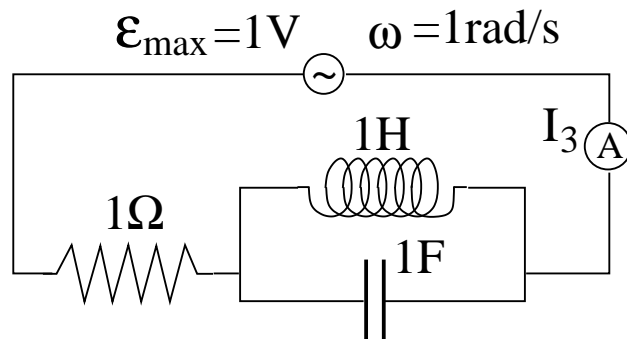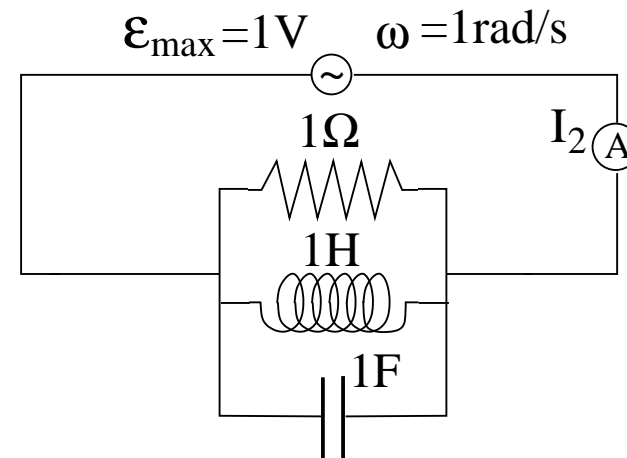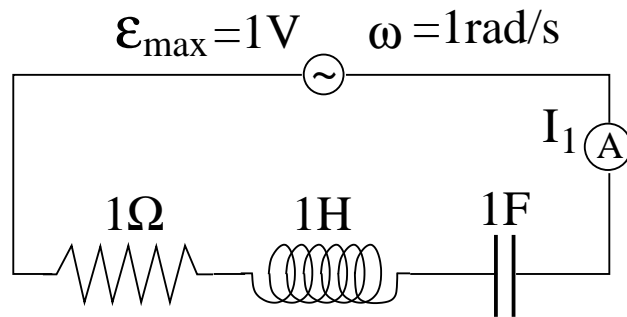
# AC Circuit Application (5)



Find the current amplitudes  $I_1, I_2, I_3, I_4$  in the four  $RLC$  circuits shown.



## AC Circuit Application (6)



Consider an  $RLC$  series circuit with inductance  $L = 88\text{mH}$ , capacitance  $C = 0.94\mu\text{F}$ , and unknown resistance  $R$ .

The ac generator  $\mathcal{E} = \mathcal{E}_{max} \sin(\omega t)$  has amplitude  $\mathcal{E}_{max} = 24\text{V}$  and frequency  $f = 930\text{Hz}$ . The phase angle is  $\delta = 75^\circ$ .



- (a) Find the resistance  $R$ .
- (b) Find the current amplitude  $I_{max}$ .
- (c) Find the maximum energy  $U_L^{max}$  stored in the inductor.
- (d) Find the maximum energy  $U_C^{max}$  stored in the capacitor.
- (e) Find the time  $t_1$  at which the current has its maximum value  $I_{max}$ .
- (f) Find the time  $t_2$  at which the charge on the capacitor has its maximum value  $Q_{max}$ .

# AC Circuit Application (7)



Consider the two ac circuits shown.

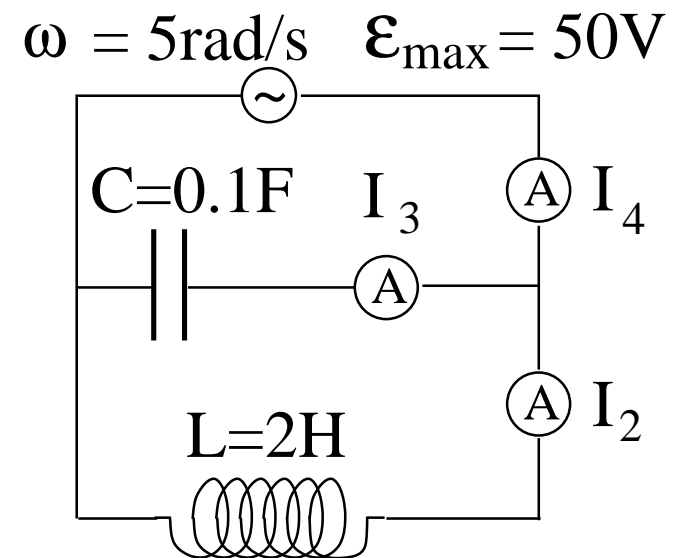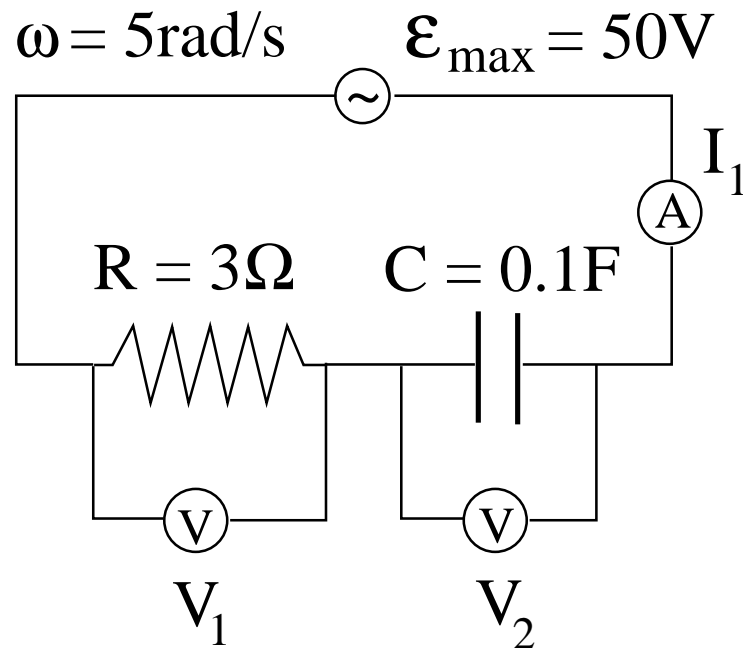- (a) In the circuit on the left, determine the current amplitude  $I_1$  and the voltage amplitudes  $V_1$  and  $V_2$ .
- (b) In the circuit on the right, determine the current amplitudes  $I_2$ ,  $I_3$ , and  $I_4$ .







# AC Circuit Application (8)



Consider the two ac circuits shown.

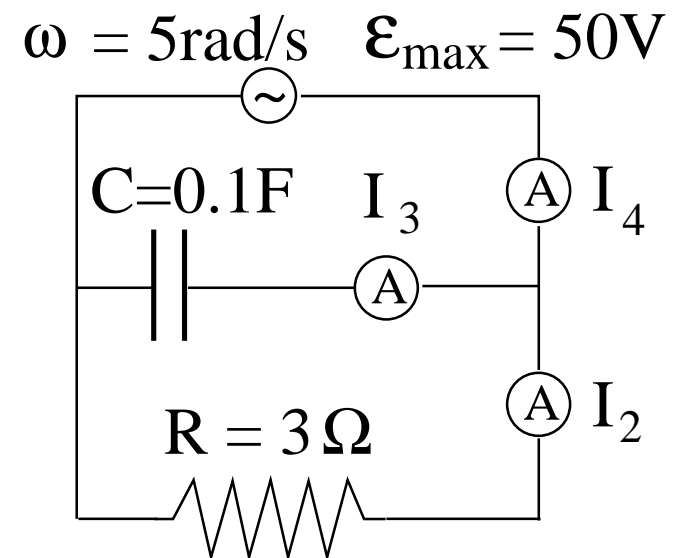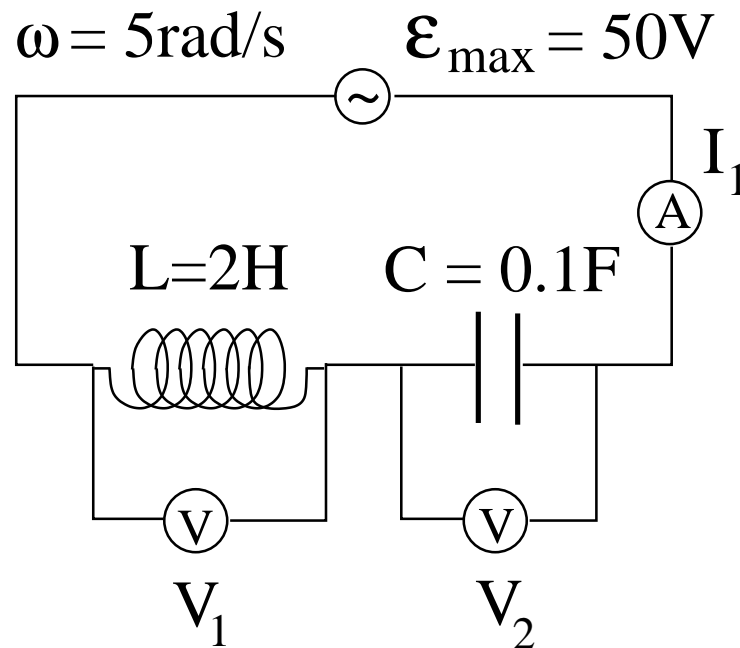- (a) In the circuit on the left, determine the maximum value of current  $I_1$  and the maximum value of voltages  $V_1$  and  $V_2$ .
- (b) In the circuit on the right, determine the maximum value of currents  $I_2$ ,  $I_3$ , and  $I_4$ .





# AC Circuit Application (9)



In the two ac circuits shown the ammeter and voltmeter readings are rms values.

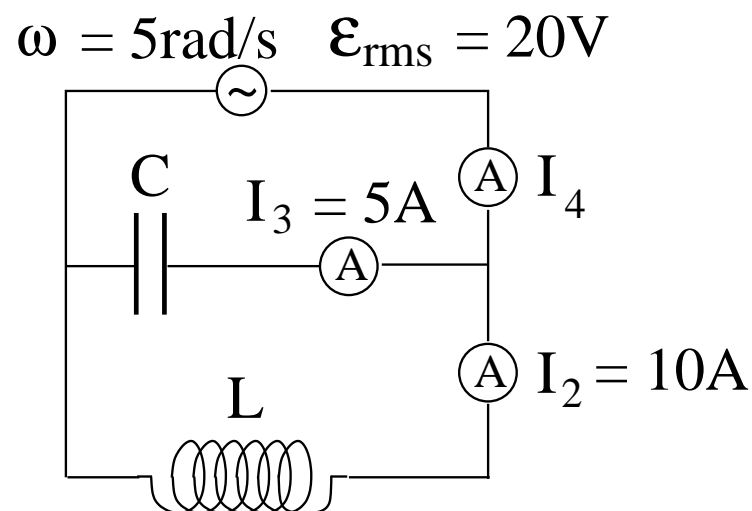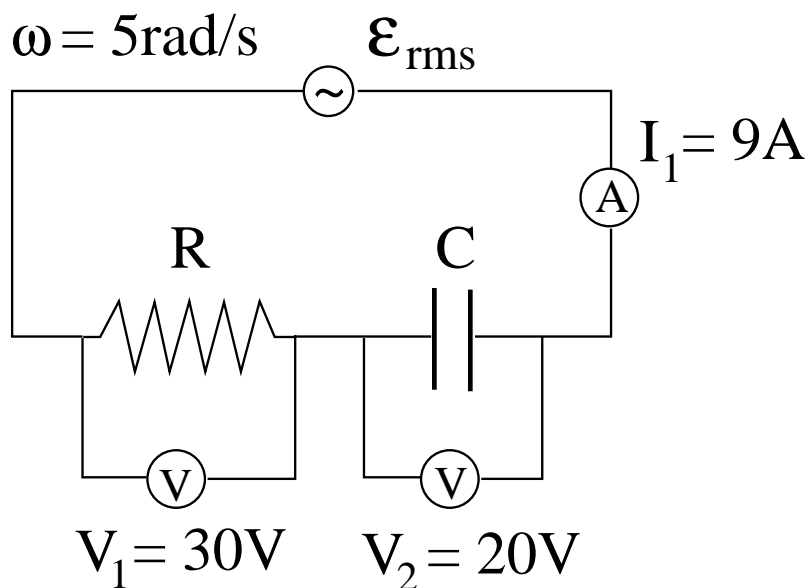- (a) In the circuit on the left, find the resistance  $R$  of the resistor, the capacitance  $C$  of the capacitor, the impedance  $Z$  of the two devices combined, and the voltage  $\mathcal{E}_{rms}$  of the power source.
- (b) In the circuit on the right, find the capacitance  $C$  of the capacitor, the inductance  $L$  of the inductor, the impedance  $Z$  of the two devices combined, and the rms value of the current  $I_4$ .



# AC Circuit Application (10)



In the two ac circuits shown the ammeter and voltmeter readings are rms values.

- (a) In the circuit on the left, find the capacitance  $C$  of the capacitor, the inductance  $L$  of the inductor, the impedance  $Z$  of the two devices combined, and the voltage  $\mathcal{E}_{rms}$  of the power source.
- (b) In the circuit on the right, find the capacitance  $C$  of the capacitor, the resistance  $R$  of the resistor, the impedance  $Z$  of the two devices combined, and the rms value of the current  $I_4$ .

