

2020

## 10. Resistor circuits. Kirchhoff's laws

Gerhard Müller  
*University of Rhode Island, gmuller@uri.edu*

Robert Coyne  
*University of Rhode Island, robcoyne@uri.edu*

Follow this and additional works at: <https://digitalcommons.uri.edu/phy204-slides>

---

### Recommended Citation

Müller, Gerhard and Coyne, Robert, "10. Resistor circuits. Kirchhoff's laws" (2020). *PHY 204: Elementary Physics II -- Slides*. Paper 35.  
<https://digitalcommons.uri.edu/phy204-slides/35>


This Course Material is brought to you by the University of Rhode Island. It has been accepted for inclusion in PHY 204: Elementary Physics II -- Slides by an authorized administrator of DigitalCommons@URI. For more information, please contact [digitalcommons-group@uri.edu](mailto:digitalcommons-group@uri.edu). For permission to reuse copyrighted content, contact the author directly.




Consider a wire with resistance  $R = \rho\ell/A$  connected to a battery.

- **Resistor rule:** In the direction of  $I$  across a resistor with resistance  $R$ , the electric potential drops:  $\Delta V = -IR$ .
- **EMF rule:** From the  $(-)$  terminal to the  $(+)$  terminal in an ideal source of emf, the potential rises:  $\Delta V = \mathcal{E}$ .
- **Loop rule:** The algebraic sum of the changes in potential encountered in a complete traversal of any loop in a circuit must be zero:  $\sum \Delta V_i = 0$ .


physical system

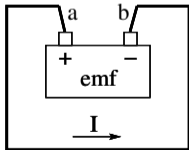

circuit diagram

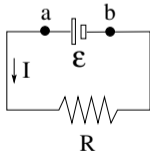




electric potential

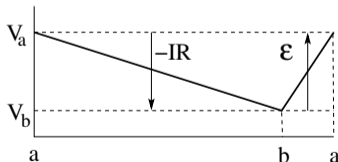
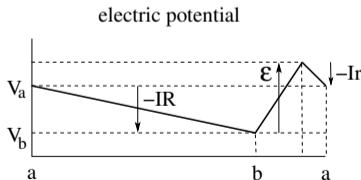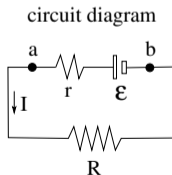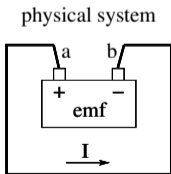
# Battery with Internal Resistance



- Real batteries have an internal resistance  $r$ .
- The terminal voltage  $V_{ba} \equiv V_a - V_b$  is smaller than the emf  $\mathcal{E}$  written on the label if a current flows through the battery.
- Usage of the battery increases its internal resistance.
- Current from loop rule:  $\mathcal{E} - Ir - IR = 0 \Rightarrow I = \frac{\mathcal{E}}{R + r}$
- Current from terminal voltage:  $V_{ba} = \mathcal{E} - Ir = IR \Rightarrow I = \frac{V_{ba}}{R}$



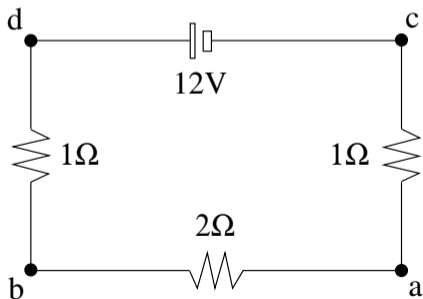
## Resistor Circuit (4)



Consider the resistor circuit shown.

- Find the direction of the positive current (cw/ccw).
- Find the magnitude of the current.
- Find the voltage  $V_{ab} = V_b - V_a$ .
- Find the voltage  $V_{cd} = V_d - V_c$ .



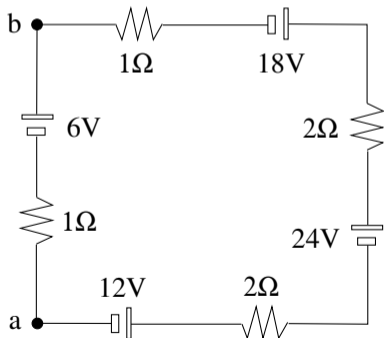
## Resistor Circuit (6)



Consider the resistor circuit shown.


- Choose a current direction and use the loop rule to determine the current.
- Name the direction of positive current (cw/ccw).
- Find  $V_{ab} \equiv V_b - V_a$  along two different paths.





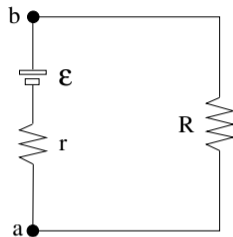
## Battery in use

- Terminal voltage:  $V_{ab} = \mathcal{E} - Ir = IR$
- Power output of battery:  $P = V_{ab}I = \mathcal{E}I - I^2r$ 
  - Power generated in battery:  $\mathcal{E}I$
  - Power dissipated in battery:  $I^2r$
- Power transferred to load:  $P = I^2R$


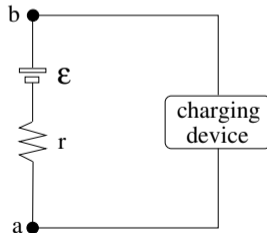
## Battery being charged:


- Terminal voltage:  $V_{ab} = \mathcal{E} + Ir$
- Power supplied by charging device:  $P = V_{ab}I$
- Power input into battery:  $P = \mathcal{E}I + I^2r$ 
  - Power stored in battery:  $\mathcal{E}I$
  - Power dissipated in battery:  $I^2r$






Consider two 24V batteries with internal resistances (a)  $r = 4\Omega$ , (b)  $r = 2\Omega$ .

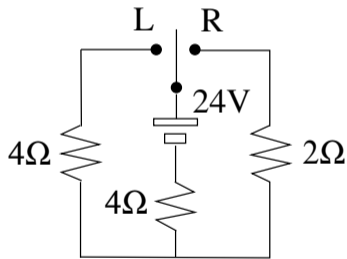- Which setting of the switch (L/R) produces the larger power dissipation in the resistor on the side?



(a)

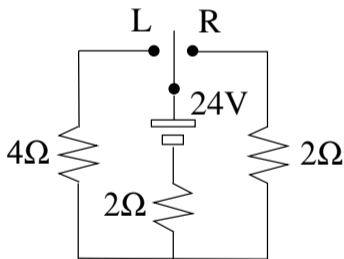



(b)



A battery providing an emf  $\mathcal{E}$  with internal resistance  $r$  is connected to an external resistor of resistance  $R$  as shown.

For what value of  $R$  does the battery deliver the maximum power to the external resistor?

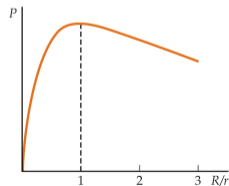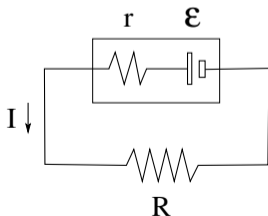- Electric current:  $\mathcal{E} - Ir - IR = 0 \Rightarrow I = \frac{\mathcal{E}}{R+r}$
- Power delivered to external resistor:  $P = I^2R = \frac{\mathcal{E}^2R}{(R+r)^2} = \frac{\mathcal{E}^2}{r} \frac{R/r}{(R/r+1)^2}$
- Condition for maximum power:  $\frac{dP}{dR} = 0 \Rightarrow R = r$





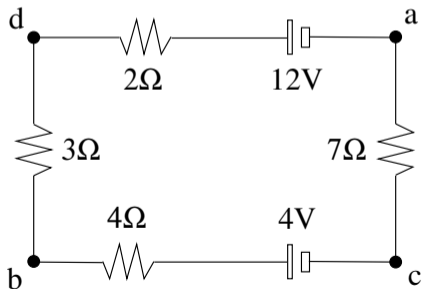
## Resistor Circuit (5)



Consider the resistor circuit shown.

- Choose a current direction and use the loop rule to determine the current.
- Name the direction of positive current (cw/ccw).
- Find the potential difference  $V_{ab} = V_b - V_a$ .
- Find the voltage  $V_{cd} = V_d - V_c$ .



# Symbols Used in Circuit Diagrams



resistor



ammeter (connect in series)



capacitor



voltmeter (connect in parallel)




inductor



diode



emf source

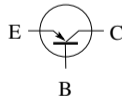


transistor



Find the equivalent resistance of two resistors connected in series.

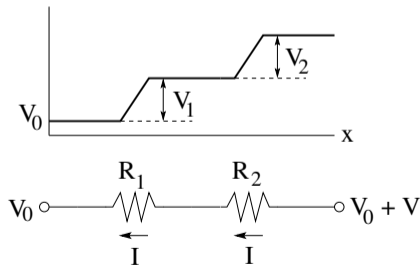- Current through resistors:  $I_1 = I_2 = I$
- Voltage across resistors:  $V_1 + V_2 = V$
- Equivalent resistance:  $R \equiv \frac{V}{I} = \frac{V_1}{I} + \frac{V_2}{I}$
- $\Rightarrow R = R_1 + R_2$





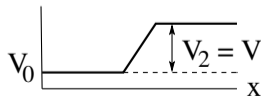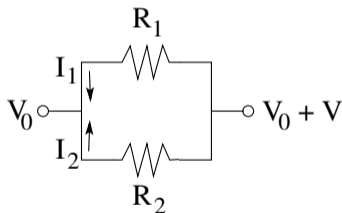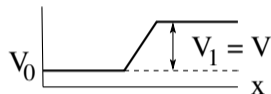
# Resistors Connected in Parallel



Find the equivalent resistance of two resistors connected in parallel.

- Current through resistors:  $I_1 + I_2 = I$
- Voltage across resistors:  $V_1 = V_2 = V$
- Equivalent resistance:  $\frac{1}{R} \equiv \frac{I}{V} = \frac{I_1}{V_1} + \frac{I_2}{V_2}$
- $\Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$





# Resistor Circuit (1)



Consider the two resistor circuits shown.

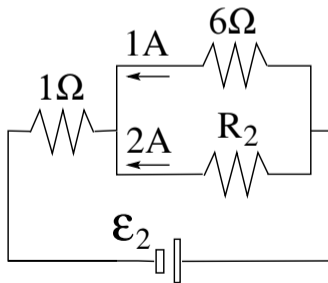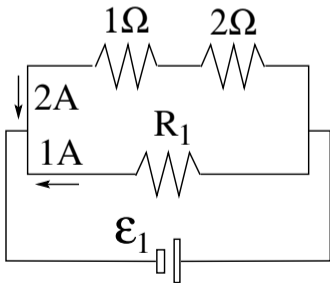- (a) Find the resistance  $R_1$ .
- (b) Find the emf  $\mathcal{E}_1$ .
- (c) Find the resistance  $R_2$ .
- (d) Find the emf  $\mathcal{E}_2$ .





## Resistor Circuit (2)



Consider the two resistor circuits shown.

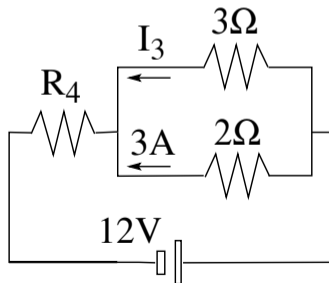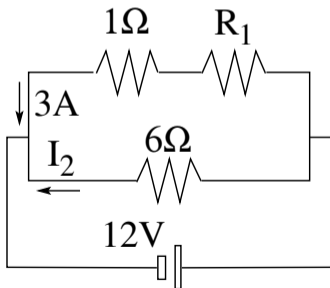- (a) Find the resistance  $R_1$ .
- (b) Find the current  $I_2$ .
- (c) Find the current  $I_3$ .
- (d) Find the resistance  $R_4$ .



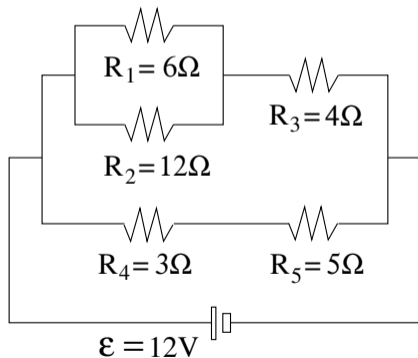
## Resistor Circuit (8)



Consider the circuit of resistors shown.

- Find the equivalent resistance  $R_{eq}$ .
- Find the currents  $I_1, \dots, I_5$  through each resistor and the voltages  $V_1, \dots, V_5$  across each resistor.
- Find the total power  $P$  dissipated in the circuit.





## Loop Rule

- When any closed-circuit loop is traversed, the algebraic sum of the changes in electric potential must be zero.

## Junction Rule

- At any junction in a circuit, the sum of the incoming currents must equal the sum of the outgoing currents.

## Strategy


- Use the junction rule to name all independent currents.
- Use the loop rule to determine the independent currents.




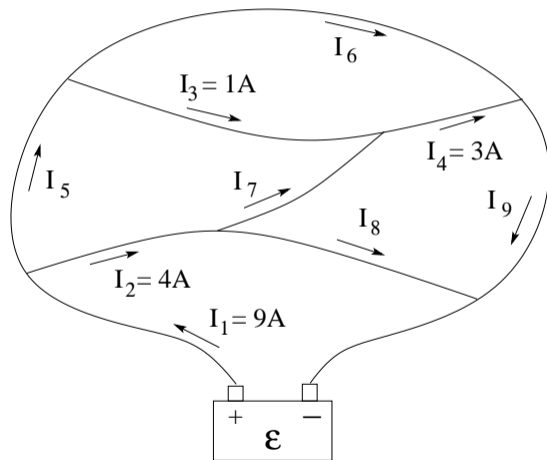
## Applying the Junction Rule

In the circuit of steady currents, use the junction rule to find the unknown currents  $I_5, \dots, I_9$ .



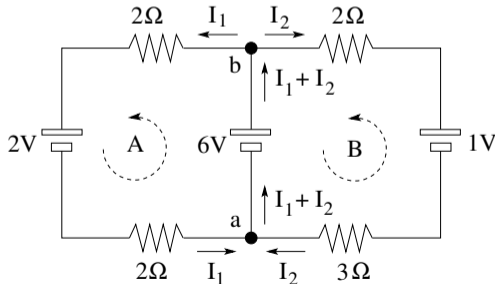
# Applying Kirchhoff's Rules



Consider the circuit shown below.

- Junction  $a$ :  $I_1, I_2$  (in);  $I_1 + I_2$  (out)
- Junction  $b$ :  $I_1 + I_2$  (in);  $I_1, I_2$  (out)
- Two independent currents require the use of two loops.
- Loop  $A$  (ccw):  $6V - (2\Omega)I_1 - 2V - (2\Omega)I_1 = 0$
- Loop  $B$  (ccw):  $(3\Omega)I_2 + 1V + (2\Omega)I_2 - 6V = 0$
- Solution:  $I_1 = 1A, I_2 = 1A$



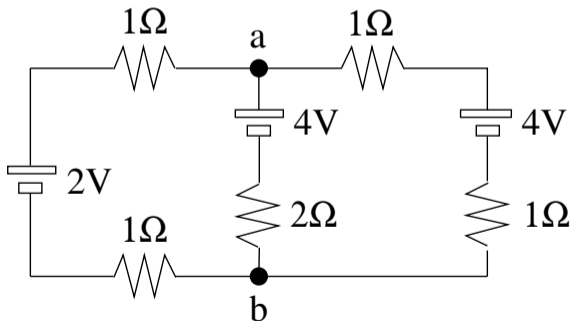
## Resistor Circuit (11)



Consider the electric circuit shown.

- Identify all independent currents via junction rule.
- Determine the independent currents via loop rule.
- Find the Potential difference  $V_{ab} = V_b - V_a$ .




## Resistor Circuit (9)



Use Kirchhoff's rules to find

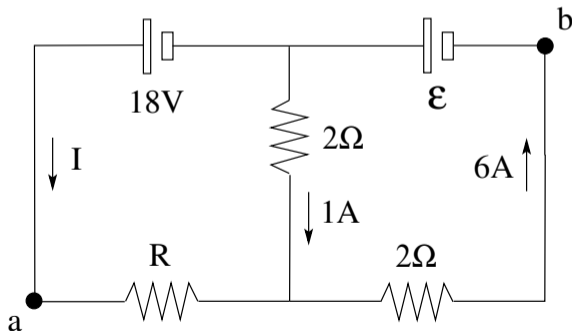- (a) the current  $I$ ,
- (b) the resistance  $R$ ,
- (c) the emf  $\mathcal{E}$ ,
- (d) the voltage  $V_{ab} \equiv V_b - V_a$ .




## Resistor Circuit (10)



Consider the electric circuit shown.

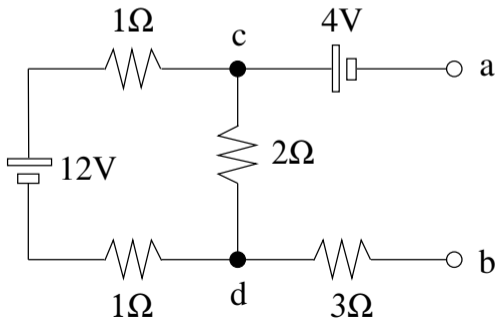- (a) Find the current through the 12V battery.
- (b) Find the current through the  $2\Omega$  resistor.
- (c) Find the total power dissipated.
- (d) Find the voltage  $V_{cd} \equiv V_d - V_c$ .
- (e) Find the voltage  $V_{ab} \equiv V_b - V_a$ .



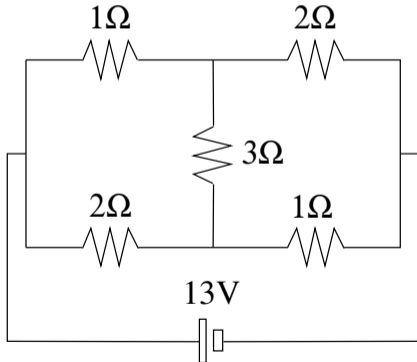
## Resistor Circuit (12)



Consider the electric circuit shown.

- Find the equivalent resistance  $R_{eq}$  of the circuit.
- Find the total power  $P$  dissipated in the circuit.



## Resistor Circuit (3)



Consider the resistor and capacitor circuits shown.

- Find the equivalent resistance  $R_{eq}$ .
- Find the power  $P_2, P_3, P_4$  dissipated in each resistor.
- Find the equivalent capacitance  $C_{eq}$ .
- Find the energy  $U_2, U_3, U_4$  stored in each capacitor.

