

University of Rhode Island

DigitalCommons@URI

PHY 204: Elementary Physics II -- Slides

PHY 204: Elementary Physics II (2021)

2020

18. RL circuits. Current buildup and shutdown

Gerhard Müller

University of Rhode Island, gmuller@uri.edu

Robert Coyne

University of Rhode Island, robcoyne@uri.edu

Follow this and additional works at: <https://digitalcommons.uri.edu/phy204-slides>

Recommended Citation

Müller, Gerhard and Coyne, Robert, "18. RL circuits. Current buildup and shutdown" (2020). *PHY 204: Elementary Physics II -- Slides*. Paper 43.

<https://digitalcommons.uri.edu/phy204-slides/43>

This Course Material is brought to you for free and open access by the PHY 204: Elementary Physics II (2021) at DigitalCommons@URI. It has been accepted for inclusion in PHY 204: Elementary Physics II -- Slides by an authorized administrator of DigitalCommons@URI. For more information, please contact digitalcommons-group@uri.edu.




Specifications:

- \mathcal{E} (emf)
- R (resistance)
- L (inductance)

Switch S :

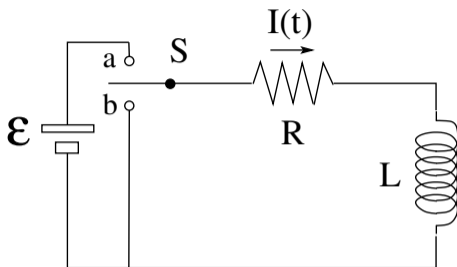- a: current buildup
- b: current shutdown





Time-dependent quantities:

- $I(t)$: instantaneous current through inductor
- $\frac{dI}{dt}$: rate of change of instantaneous current
- $V_R(t) = I(t)R$: instantaneous voltage across resistor
- $V_L(t) = L \frac{dI}{dt}$: instantaneous voltage across inductor

RL Circuit: Current Buildup in Inductor





- Loop rule: $\mathcal{E} - IR - L \frac{dI}{dt} = 0$
- Differential equation: $L \frac{dI}{dt} = \mathcal{E} - IR \Rightarrow \frac{dI}{dt} = \frac{\mathcal{E}/R - I}{L/R}$
 $\int_0^I \frac{dI}{\mathcal{E}/R - I} = \int_0^t \frac{dt}{L/R} \Rightarrow -\ln\left(\frac{\mathcal{E}/R - I}{\mathcal{E}/R}\right) = \frac{t}{L/R} \Rightarrow \frac{\mathcal{E}/R - I}{\mathcal{E}/R} = e^{-Rt/L}$
- Current through inductor: $I(t) = \frac{\mathcal{E}}{R} [1 - e^{-Rt/L}]$
- Rate of current change: $\frac{dI}{dt} = \frac{\mathcal{E}}{L} e^{-Rt/L}$

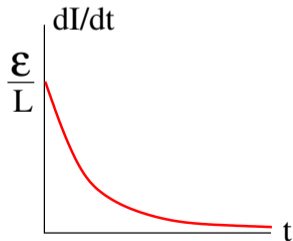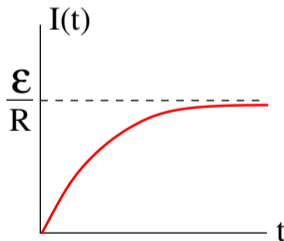

RL Circuit: Current Shutdown in Inductor



- Loop rule: $-IR - L\frac{dI}{dt} = 0$
- Differential equation: $L\frac{dI}{dt} + IR = 0 \Rightarrow \frac{dI}{dt} = -\frac{R}{L}I$
 $\Rightarrow \int_{\mathcal{E}/R}^I \frac{dI}{I} = -\frac{R}{L} \int_0^t dt \Rightarrow \ln \frac{I}{\mathcal{E}/R} = -\frac{R}{L}t \Rightarrow \frac{I}{\mathcal{E}/R} = e^{-Rt/L}$
- Current: $I(t) = \frac{\mathcal{E}}{R} e^{-Rt/L}$
- Rate of current change: $\frac{dI}{dt} = -\frac{\mathcal{E}}{L} e^{-Rt/L}$

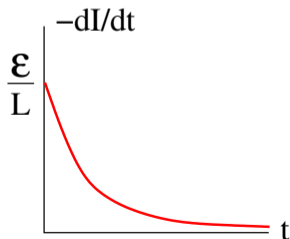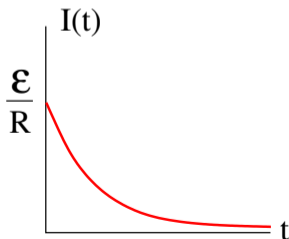


RL Circuit: Energy Transfer During Current Buildup



Loop rule: $IR + L\frac{dI}{dt} = \mathcal{E}$ ($I > 0, \frac{dI}{dt} > 0$)

- $I\mathcal{E}$: rate at which EMF source delivers energy
- $IV_R = I^2R$: rate at which energy is dissipated in resistor
- $IV_L = LI\frac{dI}{dt}$: rate at which energy is stored in inductor

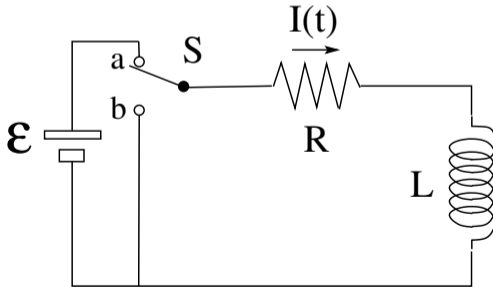Balance of energy transfer: $I^2R + LI\frac{dI}{dt} = I\mathcal{E}$




RL Circuit: Energy Transfer During Current Shutdown



Loop rule: $IR + L\frac{dI}{dt} = 0$ ($I > 0$, $\frac{dI}{dt} < 0$)

- $IV_L = LI\frac{dI}{dt}$: rate at which inductor releases energy
- $IV_R = I^2R$: rate at which energy is dissipated in resistor

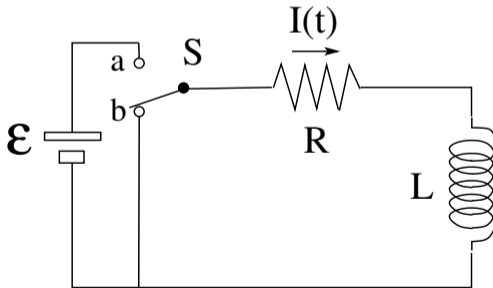
Balance of energy transfer: $I^2R + LI\frac{dI}{dt} = 0$





Specification of RL circuit
by 3 device properties:

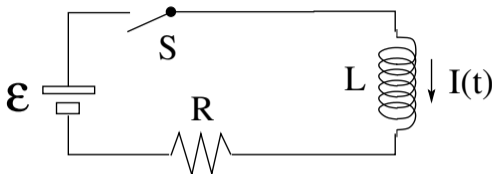- \mathcal{E} [V] (emf)
- R [Ω] (resistance)
- L [H] (inductance)



Physical properties of RL circuit during current buildup determined by 3 combinations of the device properties:

- $\frac{\mathcal{E}}{L} = \left. \frac{dI}{dt} \right|_{t=0}$: initial rate at which current increases
- $\frac{\mathcal{E}}{R} = I(t = \infty)$: final value of current
- $L/R = \tau$: time it takes to build up 63% of the current through the circuit
[$1 - e^{-1} = 0.632 \dots$]


RL Circuit: Application (8)



In the circuit shown the switch has been open for a long time.

Find the currents I_1 and I_2

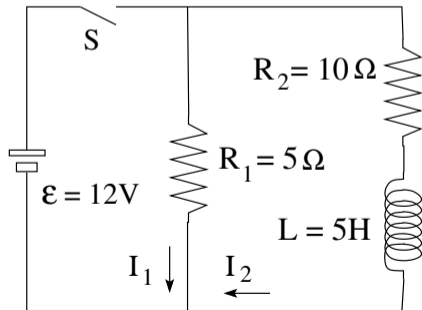- just after the switch has been closed,
- a long time later,
- as functions of time for $0 < t < \infty$.




RL Circuit: Application (7)



In the circuit shown the switch S is closed at time $t = 0$.

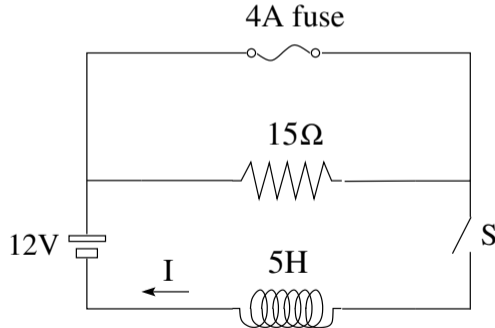- (a) Find the current I as a function of time for $0 < t < t_F$, where t_F marks the instant the fuse breaks.
- (b) Find the current I as a function of time for $t > t_F$.




RL Circuit: Application (6)



In the RL circuit shown the switch has been at position a for a long time and is thrown to position b at time $t = 0$. At that instant the current has the value $I_0 = 0.7\text{A}$ and decreases at the rate $dI/dt = -360\text{A/s}$.

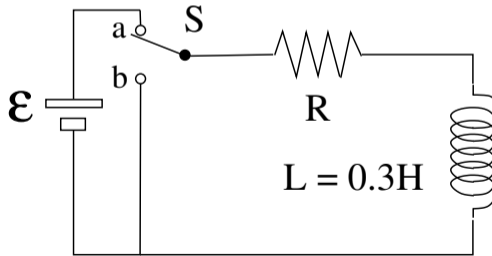- (a) Find the EMF \mathcal{E} of the battery.
- (b) Find the resistance R of the resistor.
- (c) At what time t_1 has the current decreased to the value $I_1 = 0.2\text{A}$?
- (d) Find the voltage across the inductor at time t_1 .







RL Circuit: Application (5)



Each RL circuit contains a 2A fuse. The switches are closed at $t = 0$.

- In what sequence are the fuses blown?

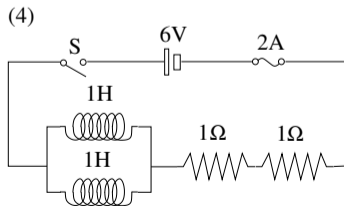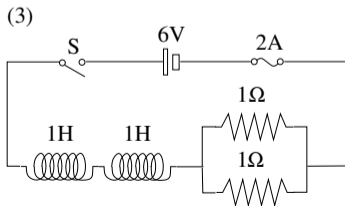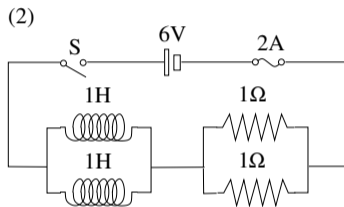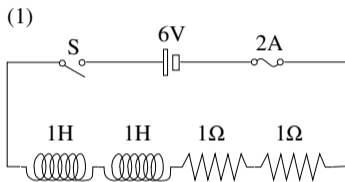

RL Circuit: Application (1)



Each branch in the circuit shown contains a 3A fuse. The switch is closed at time $t = 0$.

- (a) Which fuse is blown in the shortest time?
- (b) Which fuse lasts the longest time?

