

University of Rhode Island

DigitalCommons@URI

---

PHY 204: Elementary Physics II -- Slides

PHY 204: Elementary Physics II (2021)

---

2020

## 19. LC and RLC oscillators. Electric vs magnetic energy

Gerhard Müller

*University of Rhode Island, gmuller@uri.edu*

Robert Coyne

*University of Rhode Island, robcoyne@uri.edu*

Follow this and additional works at: <https://digitalcommons.uri.edu/phy204-slides>

---

### Recommended Citation


Müller, Gerhard and Coyne, Robert, "19. LC and RLC oscillators. Electric vs magnetic energy" (2020). *PHY 204: Elementary Physics II -- Slides*. Paper 44.

<https://digitalcommons.uri.edu/phy204-slides/44>

This Course Material is brought to you for free and open access by the PHY 204: Elementary Physics II (2021) at DigitalCommons@URI. It has been accepted for inclusion in PHY 204: Elementary Physics II -- Slides by an authorized administrator of DigitalCommons@URI. For more information, please contact [digitalcommons-group@uri.edu](mailto:digitalcommons-group@uri.edu).




- law of motion:  $F = ma$ ,  $a = \frac{d^2x}{dt^2}$
- law of force:  $F = -kx$
- equation of motion:  $\frac{d^2x}{dt^2} = -\frac{k}{m}x$
- displacement:  $x(t) = x_{max} \cos(\omega t)$
- velocity:  $v(t) = -\omega x_{max} \sin(\omega t)$
- angular frequency:  $\omega = \sqrt{\frac{k}{m}}$
- kinetic energy:  $K = \frac{1}{2}mv^2$
- potential energy:  $U = \frac{1}{2}kx^2$
- total energy:  $E = K + U = \text{const.}$

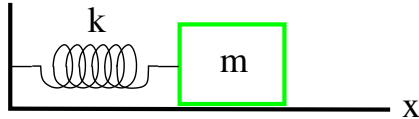




- loop rule:  $\frac{Q}{C} + L \frac{dI}{dt} = 0, I = \frac{dQ}{dt}$
- equation of motion:  $\frac{d^2Q}{dt^2} = -\frac{1}{LC}Q$
- charge on capacitor:  $Q(t) = Q_{max} \cos(\omega t)$
- current through inductor:  $I(t) = -\omega Q_{max} \sin(\omega t)$
- angular frequency:  $\omega = \frac{1}{\sqrt{LC}}$
- magnetic energy:  $U_B = \frac{1}{2}LI^2$  (stored on inductor)
- electric energy:  $U_E = \frac{Q^2}{2C}$  (stored on capacitor)
- total energy:  $E = U_B + U_E = \text{const.}$

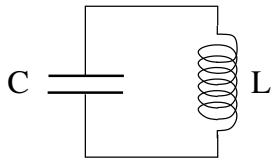



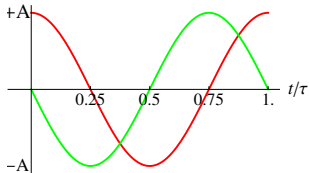
## mechanical oscillations

- position:  $x(t) = A \cos(\omega t)$  [red]
- velocity:  $v(t) = -A \sin(\omega t)$  [green]
- period:  $\tau = \frac{2\pi}{\omega}$ ,  $\omega = \sqrt{\frac{k}{m}}$



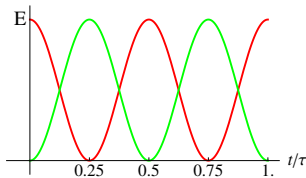- potential energy:  $U(t) = \frac{1}{2}kx^2(t)$  [r]
- kinetic energy:  $K(t) = \frac{1}{2}mv^2(t)$  [g]
- total energy:  $E = U(t) + K(t) = \text{const}$



## electromagnetic oscillations


- charge:  $Q(t) = A \cos(\omega t)$  [red]
- current:  $I(t) = -A \sin(\omega t)$  [green]
- period:  $\tau = \frac{2\pi}{\omega}$ ,  $\omega = \frac{1}{\sqrt{LC}}$

- electric energy:  $U_E(t) = \frac{1}{2C}Q^2(t)$  [r]
- magnetic energy:  $U_B(t) = \frac{1}{2}LI^2(t)$  [g]
- total energy:  $E = U_E(t) + U_B(t) = \text{const}$
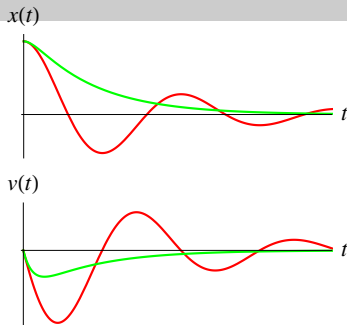
# Mechanical Oscillator with Damping



- law of motion:  $F = ma$ ,  $a = \frac{d^2x}{dt^2}$
- law of force:  $F = -kx - bv$ ,  $v = \frac{dx}{dt}$
- equation of motion:  $\frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{k}{m} x = 0$



Solution for initial conditions  $x(0) = A$ ,  $v(0) = 0$ :

(a) **underdamped motion:**  $b^2 < 4km$

$$x(t) = Ae^{-bt/2m} \left[ \cos(\omega't) + \frac{b}{2m\omega'} \sin(\omega't) \right] \quad \text{with} \quad \omega' = \sqrt{\frac{k}{m} - \frac{b^2}{4m^2}}$$



(b) **overdamped motion:**  $b^2 > 4km$

$$x(t) = Ae^{-bt/2m} \left[ \cosh(\Omega't) + \frac{b}{2m\Omega'} \sinh(\Omega't) \right] \quad \text{with} \quad \Omega' = \sqrt{\frac{b^2}{4m^2} - \frac{k}{m}}$$
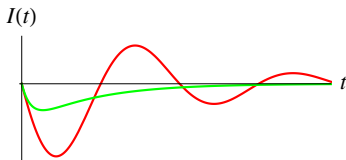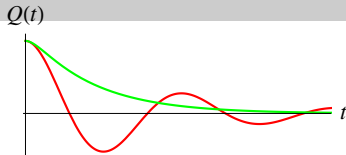
# Damped Electromagnetic Oscillator (RLC Circuit)



- loop rule:  $RI + L \frac{dI}{dt} + \frac{Q}{C} = 0, I = \frac{dQ}{dt}$
- equation of motion:  $\frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC}Q = 0$



Solution for initial conditions  $Q(0) = Q_{max}, I(0) = 0$ :

(a) **underdamped motion:**  $R^2 < \frac{4L}{C}$

$$Q(t) = Q_{max} e^{-Rt/2L} \left[ \cos(\omega't) + \frac{R}{2L\omega'} \sin(\omega't) \right] \quad \text{with} \quad \omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

(b) **overdamped motion:**  $R^2 > \frac{4L}{C}$

$$Q(t) = Q_{max} e^{-Rt/2L} \left[ \cosh(\Omega't) + \frac{R}{2L\Omega'} \sinh(\Omega't) \right] \quad \text{with} \quad \Omega' = \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$


# Oscillator with Two Modes



Electromagnetic:


$$\text{mode \#1: } L \frac{dI}{dt} + \frac{Q}{C} + \frac{Q}{C} + L \frac{dI}{dt} = 0, \quad I = \frac{dQ}{dt}$$
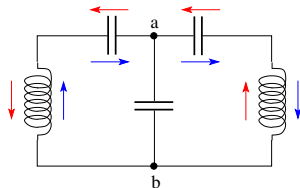
$$\Rightarrow \frac{dI}{dt} = -\frac{Q}{LC} \Rightarrow \frac{d^2Q}{dt^2} = -\omega^2 Q, \quad \omega = \frac{1}{\sqrt{LC}}$$



$$\text{mode \#2: } L \frac{dI}{dt} + \frac{Q}{C} + \frac{2Q}{C} = 0, \quad I = \frac{dQ}{dt}$$

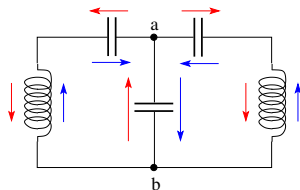
$$\Rightarrow \frac{dI}{dt} = -\frac{3Q}{LC} \Rightarrow \frac{d^2Q}{dt^2} = -\omega^2 Q, \quad \omega = \sqrt{\frac{3}{LC}}$$



Mechanical:

$$\text{mode \#1: } \omega = \sqrt{\frac{k}{m}}$$
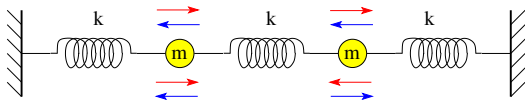
$$\text{mode \#2: } \omega = \sqrt{\frac{3k}{m}}$$



# RLC Circuit: Application (1)



In the circuit shown the capacitor is without charge.

When the switch is closed to position *a*...


(a) find the initial rate  $dI/dt$  at which the current increases from zero,

(b) find the charge  $Q$  on the capacitor after a long time.

Then, when the switch is thrown from *a* to *b*...

(c) find the time  $t_1$  it takes the capacitor to fully discharge,

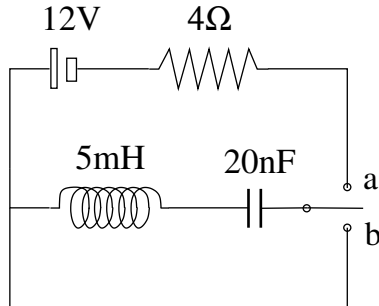(d) find the maximum current  $I_{max}$  in the process of discharging.





## RLC Circuit: Application (2)



In the circuit shown the capacitor is without charge and the switch is in position *a*.


(i) When the switch is moved to position *b* we have an *RL* circuit with the current building up gradually:

$$I(t) = (\mathcal{E}/R)[1 - e^{-t/\tau}].$$

Find the time constant  $\tau$  and the current  $I_{max}$  after a long time.

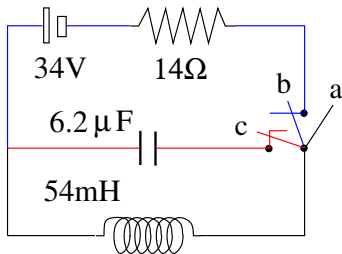(ii) Then we reset the clock and move the switch from *b* to *c* with no interruption of the current through the inductor. We now have a an *LC* circuit:  $I(t) = I_{max} \cos(\omega t)$ .

Find the angular frequency of oscillation  $\omega$  and the maximum charge  $Q_{max}$  that goes onto the capacitor periodically.



## RLC Circuit: Application (3)



In the circuit shown the capacitor is without charge and the switch is in position *a*.


(i) When the switch is moved to position *b* we have an *RC* circuit with the capacitor being charged up gradually:  $Q(t) = \mathcal{E}C[1 - e^{-t/\tau}]$ .

Find the time constant  $\tau$  and the charge  $Q_{max}$  after a long time.

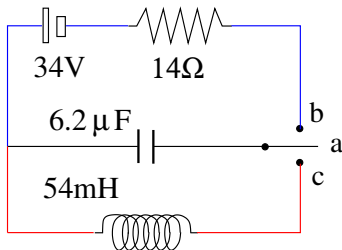(ii) Then we reset the clock and move the switch from *b* to *c*.

We now have a an *LC* circuit:  $Q(t) = Q_{max} \cos(\omega t)$ .





Find the angular frequency of oscillation  $\omega$  and the maximum current  $I_{max}$  that flows through the inductor periodically.


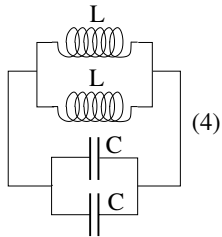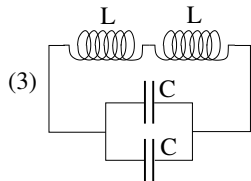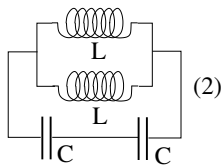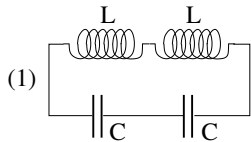
# LC Circuit: Application (1)



Name the  $LC$  circuit with the highest and the lowest angular frequency of oscillation.



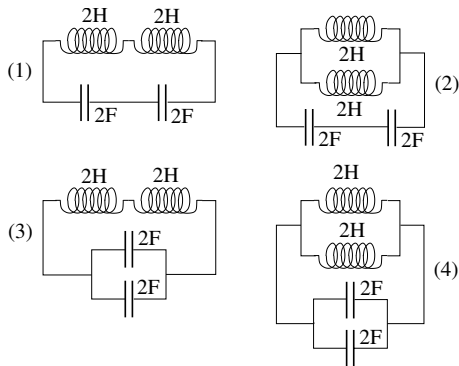
## LC Circuit: Application (2)



At time  $t = 0$  a charge  $Q = 2C$  is on each capacitor and all currents are zero.

- What is the energy stored in the circuit?
- At what time  $t_1$  are the capacitors discharged for the first time?
- What is the current through each inductor at time  $t_1$ ?



# LC Circuit: Application (3)



In these  $LC$  circuits all capacitors have equal capacitance  $C$  and all inductors have equal inductance  $L$ . Sort the circuits into groups that are equivalent.

